

AC Power


April 21, 2020 1:13 PM

Power
 - (+) if power absorbed
 - (-) if power supplied

Instantaneous Power: $p(t) = v(t) \cdot i(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$
Average Power: $P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$

Power Formulas

Complex Power: $S = P + jQ = V_{rms} \cdot I_{rms}^* = V_{rms} I_{rms} \angle \theta_v - \theta_i$
Apparent Power: $|S| = V_{rms} I_{rms} = \sqrt{P^2 + Q^2}$
Real Power: $P = \text{Re}(S) = S \cos(\theta_v - \theta_i)$
Reactive Power: $Q = \text{Im}(S) = S \sin(\theta_v - \theta_i)$
Power Factor: $P/S = \cos(\theta_v - \theta_i)$

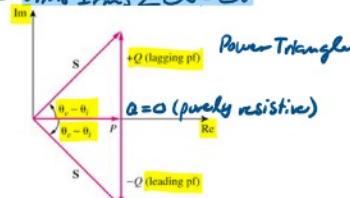

Power Factor

- Power factor: $PF = \cos(\theta_v - \theta_i)$
- lagging: $0 < PF < 1 \rightarrow [0, 90^\circ]$ (+)
- leading: $0 < PF < 1 \rightarrow [-90^\circ, 0]$ (-)
- @ -90° : $PF = 0$, pure reactive/capacitive, no real power consumption
- @ 90° : $PF = 0$, pure reactive/inductive, no real power consumption

Complex Power

$S = \frac{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}{P} + j \frac{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}{Q}$
S → avg power delivered to load
Q → reactive power exchange b/w source & reactive part of load
 L { Resistive load (PF=1) $Q=0$
 Capacitive load (leading PF) $Q < 0$
 Inductive load (lagging PF) $Q > 0$

Power Factor Correction

- Increasing the power factor w/o altering the voltage/current to original load
- Conservation of AC Power: $S = UI^* = V I_1^* + V I_2^*$



- Add capacitor in parallel to loads
 - Capacitor receives (-) reactive power
ex. For 2 loads: Total $P = 2.4 \text{ kW}$, $PF = 0.8$ lagging, $\omega = 60 \text{ Hz}$
 Apparent power: $S = P/PF = 3 \text{ kVA}$
 $\theta = \cos^{-1}(0.8) = 36.87^\circ$
 $S = S \angle \theta = 3 \angle 36.87^\circ \text{ kVA}$
 Load 1: $S_1 = P_1/PF_1 = 2.122 \text{ kVA}$
 $PF_1 \rightarrow \theta_1 = 45^\circ (1.43)$
 $S = S_1 \angle \theta_1 = 2.122 \angle 45^\circ \text{ kVA}$
 Load 2: Power conservation: $S_2 = S - S_1 = 0.948 \angle 18.42^\circ \text{ kVA}$
 $PF_2 = \cos(18.42) = 0.944$ (lag)


Power Factor Correction: Total Reactive Power: $Q_1 + Q_2 = 1.8 \text{ kVAR}$
 - Add capacitor in parallel: $Q_c = -(Q_1 + Q_2) = -1.8 \text{ kVAR}$
 - Complex Power received by capacitor: $S_c = -j\omega |V|^2 = jQ_c$
 $\rightarrow C = \frac{Q_c}{\omega |V|^2} = \frac{1.8 \times 10^3}{2\pi \cdot 60 \cdot 120^2} = 331.6 \mu\text{F}$

★ Workbook ST2

Navigation sidebar for the workbook problem set.

ST2: Problem 3

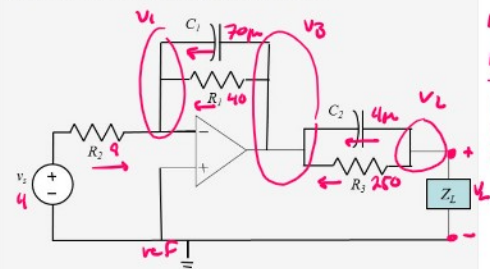(10 points)
 Let $v_s(t) = 4\cos(377t) \text{ V}$, $R_1 = 40\Omega$, $R_2 = 90\Omega$, $R_3 = 250\Omega$, $C_1 = 70\mu\text{F}$ and $C_2 = 4\mu\text{F}$. Determine the complex load Z_L to maximize the average power it receives and compute the resulting values for the load. When writing the power as a function of time, write the phase as an angle between -90 and 90 degrees.



Note: Use "j" when submitting complex and imaginary numbers (e.g. submit $4+j3$ for a complex number with real component 4 and imaginary component 3)

!!

★ To Maximize Avg power to Z_L , $Z_L = Z_{th}^* = \left(\frac{V_{th}}{I_{sc}}\right)^*$

Thevenin w/ op-amp: 1A/2A test

1A Source: $S = 377j$

$$KCL1: \frac{4-v_1}{9} + \frac{v_2-v_1}{40} + \frac{v_1-v_2}{250} = 0$$

2A Source: $S = 377j$

$$A \rightarrow 2A \text{ source} \rightarrow 30.2498 - 287.754029j$$

$$KCL2: I = \frac{v_2-v_3}{40} + \frac{v_2-v_3}{250}$$

$$NF: v_1 = 0 \rightarrow \text{solve } v_{2A} = 53.9198 - 139.439068j$$

$$\begin{bmatrix} 1 & 1 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} V_{th} \\ I_{sc} \end{bmatrix} = \begin{bmatrix} V_{th} \\ V_{th} \end{bmatrix} \rightarrow R_{th} =$$

Z_L maximized when $Z_L = Z_{th}^*$

$$53.9198 - 139.439068j$$

$$116.24798 - 287.754029j$$

○

Note: Use "j" when submitting complex and imaginary numbers (e.g. submit 4+j3 for a complex number with real component 4 and imaginary component 3)

a. Impedance, $Z_L =$ Ω

b. Apparent power received, $S =$ VA

c. Average power received, $P =$ W

d. Reactive power received, $Q =$ VAR

e. Complex power received, $S =$ VA

f. Instantaneous power received $p(t) =$ + $\cos(754t +$ $^\circ)$ W

$$S = 3.7178 - j0.737068j$$


$$116.24798 - 287.754029j$$



ST2: Problem 4

Previous Problem Problem List Next Problem

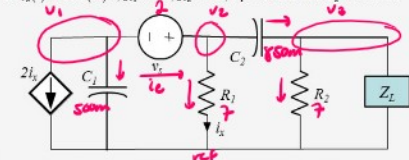(10 points)
Let $v_s(t) = 2\cos(2t)$ V, $R_1 = 7\Omega$, $R_2 = 7\Omega$, $C_1 = 500\text{mF}$ and $C_2 = 850\text{mF}$.



Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)


- a. If Z_L is a purely resistive load chosen to maximize the average power it receives, the resistor value is $Z_L =$ Ω and the resulting average power is $P =$ W.
- b. If Z_L is a complex load chosen to maximize the average power it receives, the load value is $Z_L =$ + j Ω and the resulting average power is $P =$ W.

$$Z_{CL} = 0 = 2j\omega$$

ST2: Problem 5

Previous Problem Problem List Next Problem

(10 points)
In the diagram below, the source voltage phasor is $V_s = 120\angle 30^\circ$ V (rms) and measurements show that Plant 1 receives 36kW with PF 0.6 leading, plant 2 receives 65kW with PF 0.8 lagging and Plant 3 receives 65kW with PF 0.9 lagging. Compute the current phasor I_o and the overall power factor. If the source frequency is 60Hz, what single passive (time domain) component value should be added in parallel to bring the power factor to unity?

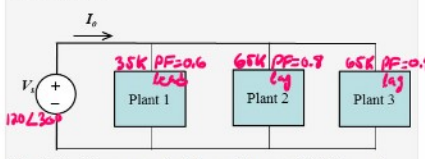

Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

$I_o =$ \angle $^\circ$ A (rms)

Overall PF: ?

Component: ?

a) Load 1: $S_{11} = \frac{P_1}{\text{pf}} = \frac{35}{0.6} = 58.333\text{ kVA}$
 $\theta_1 = \cos^{-1}(0.6) = -53.13010$
 $I_1 = 58.333 \angle -53.13010 = (120 \angle 30^\circ)(I_{rms1})^*$
 $I_1 = 486.1111 \angle 83.1301^\circ$

Load 2: $S_2 = 81.25 \angle 36.8699^\circ \text{ kVA}$
 $I_2 = 677.0835 \angle -6.16181^\circ$

Load 3: $S_3 = 72.2222 \angle 25.84183^\circ$
 $I_3 = 601.8585 \angle 4.15806^\circ$

$I_o = I_1 + I_2 + I_3 =$
 $\text{b) } \text{pf} = \cos(\theta_o - \theta_i) = \cos(30^\circ - 18.50178^\circ) = 0.979931 \text{ (lag)}$
 c) Reactive power $Q = Q_1 + Q_2 + Q_3$ $\omega = 120\pi$

$$Q_C = \frac{|V|^2}{Z_C} = \frac{|V|^2}{1/j\omega C}$$

$$C = \frac{Q_C}{-\omega|V|^2} =$$

ST2: Problem 6

Previous Problem Problem List Next Problem


(10 points)
Consider a voltage source, $v_s(t) = 120\sqrt{2}\cos(377t)$ V, connected across two loads in series ($v_{s1} = v_1 + v_2$). If the load voltmeter RMS readings measure 85V and 51.75V, respectively, with the voltage of the first load leading that of the second (by an angle between 0 and 180 degrees), determine the phases for v_1 and v_2 . If you also know that load 1 has PF 0.9 lagging, compute the PF of load 2.

Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

a. Phase of $v_1(t)$: $^\circ$

b. Phase of $v_2(t)$: $^\circ$

c. Load 2 PF: ?

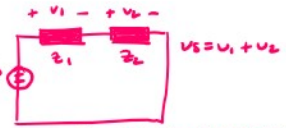

$120\angle 0^\circ = 85\angle \theta_1 + 51.75\angle \theta_2$
 $\text{Re(1): } 120 = 85\cos(\theta_1) + 51.75\cos(\theta_2)$
 $\text{Im(1): } 0 = 85\sin(\theta_1) + 51.75\sin(\theta_2)$
 $\rightarrow \text{solve: } \theta_1 = -37.5029^\circ = \theta_{v1}$
 $\theta_2 = 21.75587^\circ = \theta_{v2}$
 $Z_1: 0.9 = \cos(\theta_v - \theta_i) \rightarrow \theta_v - \theta_i = 25.84193^\circ$
 $\theta_i = \theta_{v1} - (\theta_v - \theta_i) = -4.086054^\circ \rightarrow \theta_{i1} = \theta_{i2}$
 $Z_2: \theta_v - \theta_i = \theta_{v2} - \theta_{i2} = -33.41684^\circ$
 $\text{pf}_2 = \cos(\theta_v - \theta_i) = 0.83468 \text{ leading}$



ST2: Problem 7

Previous Problem Problem List Next Problem

(10 points)
In the quasi-stationary electric power system in the figure, a voltmeter reads the same at the source and at the load, 128 volts. At the source, an ammeter reads 28 amps. The source sees a capacitive circuit. The cable (feeder) has a resistance of 0.276482 ohms and a reactance of 1.108915 ohms. (a) What is the power factor angle, in degrees, at the source? (b) What is the active power delivered by the source? (c) What is the reactive power delivered by the source? (d) What is the power factor angle at the load, in degrees? (e) What is the active power absorbed by the load? (f) What is the reactive power absorbed by the load.


Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

Simple Power System

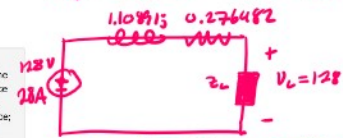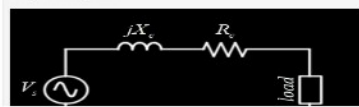

$V_s \angle \theta_s = V_{th} \angle \theta_{Vth} + V_L \angle \theta_{VL} = I_{rms} \cdot Z_{th} + 128 \angle \theta_{VL}$
 $128 \angle \theta_s = (28)(0.276482 + j1.108915) + 128 \angle \theta_{VL}$
 $V_s \angle \theta_s = V_s \cos(\theta_s) + jV_s \sin(\theta_s)$
 $128 \cos(\theta_s) + j128 \sin(\theta_s) = 7.741496 + 31.04948j + 128 \cos(\theta_{VL}) + j128 \sin(\theta_{VL})$
 $\text{Re(1): } 128 \cos(\theta_s) = 7.741496 + 128 \cos(\theta_{VL})$
 $\text{Im(1): } 128 \sin(\theta_s) = 31.04948 + 128 \sin(\theta_{VL})$
 $\rightarrow \text{solve: } \theta_s = -6.8192254^\circ \rightarrow \text{pf angle @ source}$
 $\theta_{VL} = -21.1807438^\circ$
 $\text{b) } |S| = V_{rms} \cdot I_{rms} = (128)(28) = 3584 \text{ VA}$

Problem 7
Problem 8
Problem 9
Problem 10

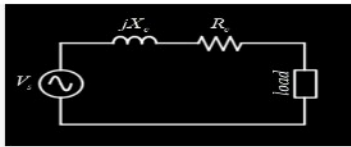

- (a) $\theta_s =$ deg
(b) $P_s =$ W
(c) $Q_s =$ VAR
(d) $\theta_f =$ deg
(e) $P_f =$ W
(f) $Q_f =$ VAR

ST2: Problem 9


Previous Problem Problem List Next Problem

(10 points)

In the figure, the load absorbs 14.336 kVA at a power factor 0.891007 Inductive. For the feeder (cable) $R = 0.27 \text{ ohms}$, and $X = 3 \Omega$. The voltage at the source is 265.713 volts. What is the voltage at the load, in volts?


Note: In this problem, you may only submit numerical answers, (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

Simple Power System

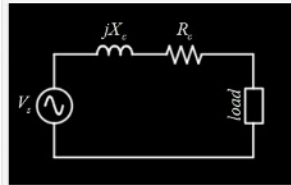

$V_{\text{load}} =$ V

- $2-1$: $128 \sin(\theta_s) = 31.04448 + 128 \sin(\theta_v)$
a) \rightarrow solve: $\theta_s = -6.8192254^\circ \rightarrow$ pf angle @ source
d) $\theta_v = -21.1807438^\circ$
b) $|S| = V_{\text{rms}} \cdot I_{\text{rms}} = (128)(25) = 3584 \text{ VA}$
 $P = P_e(S) = |S| \cos(\theta_v - \theta_i) = 3584 \cos(-6.8192254^\circ) = 3558.645788 \text{ W}$
c) $Q = Q_e(S) = |S| \sin(\theta_v - \theta_i) = 3584 \sin(-6.8192254^\circ) = -425.5539376 \text{ VAR}$
e) $P = P_e(S) = |S| \cos(\theta_v - \theta_i) = 3584 \cos(-21.1807438^\circ) = 3341.8839 \text{ W}$
f) $Q = Q_e(S) = |S| \sin(\theta_v - \theta_i) = 3584 \sin(-21.1807438^\circ) = -1294.4393783 \text{ VAR}$

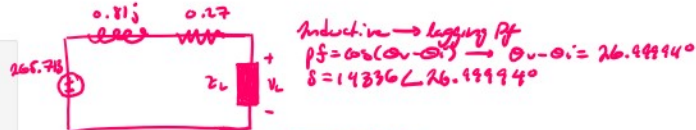

Inductive \rightarrow lagging pf
 $pf = \cos(\theta_v - \theta_i) \rightarrow \theta_v - \theta_i = 26.99994^\circ$
 $\delta = 14336 \angle 26.99994^\circ$

- $265.713 \angle 0^\circ = I_{\text{rms}} \cdot Z_{\text{th}} + V_L \angle \theta_L$
 $265.713 \cos(\theta_v) + 265.713 j \sin(\theta_v) = I_{\text{rms}}(0.27 + j0.81) + V_L \cos(26.99994^\circ) + j V_L \sin(26.99994^\circ)$
1) Real: $265.713 \cos(\theta_v) = I_{\text{rms}}(0.27) + V_L \cos(26.99994^\circ)$
2) Imag: $265.713 \sin(\theta_v) = I_{\text{rms}}(0.81) + V_L \sin(26.99994^\circ)$
 $|S| = V_{\text{rms}} \cdot I_{\text{rms}}$
 $14336 = V_L \cdot I_{\text{rms}}$
 \rightarrow solve: $V_L = 724 \text{ V}$

ST2
Problem 9
User Settings
Credits

Problems

Problem 1
Problem 2
Problem 3
Problem 4
Problem 5
Problem 6
Problem 7
Problem 8
Problem 9
Problem 10

Homework
Site
ST2
Problem 10
User Settings
Credits

Problems

Problem 1
Problem 2
Problem 3
Problem 4
Problem 5
Problem 6
Problem 7
Problem 8
Problem 9
Problem 10

ST2: Problem 10


Previous Problem Problem List Next Problem

(10 points)


In the figure, a 337.38 volts source delivers 16.5316 kVA at a power factor 0.715683 Inductive through a cable with $R = 0.12 \text{ ohms}$ and $X = 4 \Omega$ to a load. Compute: (a) the voltage at the load, (b) the active power of the load, (c) the reactive power of the load and (d) the power factor angle of the load.

Note: In this problem, you may only submit numerical answers, (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

Simple Power System

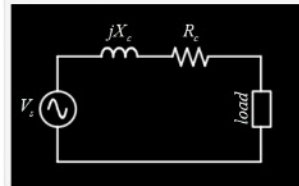

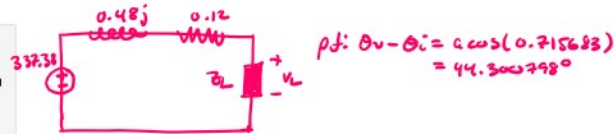$V_{\text{load}} =$ V
 $P_{\text{load}} =$ W
 $Q_{\text{load}} =$ VAR
 $\theta_{\text{load}} =$ deg



pf: $\theta_v - \theta_i = \cos(0.715683)$
 $= 44.300798^\circ$

- a) Apparent Power: $16531.6 = 337.38 \cdot I_{\text{rms}} \rightarrow I_{\text{rms}} = 48.99994 \text{ A}$
 $337.38 \angle 44.300798^\circ = (48.99994)(0.12 + j0.48) + V_L \angle \theta_L$
 $V_L \angle \theta_L = V_L \cos(\theta_v) + j V_L \sin(\theta_v)$
 $241.457132 + 235.6347j = 5.87999 + 23.51997j + V_L \cos(\theta_v) + j V_L \sin(\theta_v)$
Real: $241.457132 = 5.87999 + V_L \cos(\theta_v)$
Imag: $235.6347 = 23.51997 + V_L \sin(\theta_v)$
 \rightarrow solve: $V_L = 317.00039 \text{ V}$
 $\theta_v = 42^\circ$