

# Resonance


February 15, 2020 9:33 AM

## LC circuit



- frequency of resonance:  $\omega_0 = \frac{1}{\sqrt{LC}}$
- LC circuit looks & behaves like short circuit


## RLC circuits

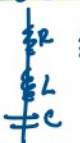

- @ resonance  $\omega_0$ , L & C cancel out
- RLC series behaves as resistance
- $Z_T = \frac{LC\omega^2 + RC\omega + 1}{C\omega} \rightarrow \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC}$

## Amplitude of Bode Plot

- Impedance of series RLC:

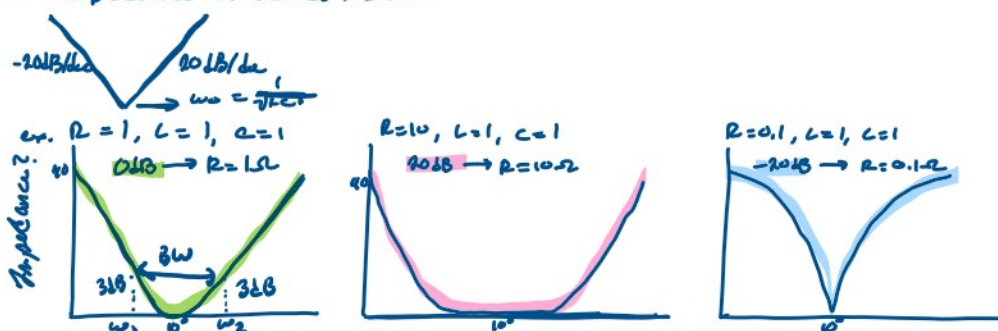

- Bandwidth:  $BW = \omega_2 - \omega_1 \rightarrow$  Half power frequencies

- Quality Factor:  $Q = \frac{\omega_0}{BW}$

## RLC Series

- ex. If impedance  $\rightarrow$  3dB higher:  $20 \log \left( \frac{Z_{3dB}}{Z_n} \right) = 3$ ,  $Z_{3dB} = Z_n \sqrt{2}$
- $Z_n = R$ , what freq  $\omega_0$  does this happen?

$$\sqrt{2} R = \sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$$

$\rightarrow$  2 quadratic eqns in  $\omega$ , each w/ 2 roots, take positive of each

$$\textcircled{1} \omega_1^2 LC - \omega_1 RC - 1 = 0$$

$$\omega_1 = \frac{RC + \sqrt{(RC)^2 + 4LC}}{2LC} \rightarrow \text{greater: } \omega_1$$

$$\textcircled{2} \omega_2^2 LC + \omega_2 RC - 1 = 0$$


$$\omega_2 = \frac{-RC + \sqrt{(RC)^2 + 4LC}}{2LC} \rightarrow \text{smaller: } \omega_2$$

$$BW = \omega_2 - \omega_1 = \frac{R}{L}$$

$$Q = \frac{\omega_0}{BW} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$\}$  ONLY for RLC series

## RLC Parallel

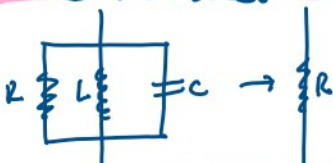

- @ resonant frequency, behaves just like R

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 RC = \frac{R}{\omega_0 L} = R \sqrt{\frac{C}{L}}$$

$$BW = \omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

$\}$  ONLY for RLC parallel

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$BW = \omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

∴ For Series & parallel Half power  $\omega_{1,2}$ :  $\omega_{1,2} = \omega_0 \left[ \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{1}{2Q} \right]$

### Scaling Recipes

- Filter "cookbooks"
- Scale filters for different components

### Frequency Scaling

- Want same impedance  $Z$  but at  $k_f$  times original  $f$

need new values for  $L'$  &  $C'$

$$Z_L = j\omega k_f L' = j\omega L \rightarrow L' = \frac{L}{k_f}$$

$$Z_C = \frac{1}{j\omega k_f C'} = \frac{1}{j\omega C} \rightarrow C' = \frac{C}{k_f}$$

Higher frequencies  
but same impedance

∴ Divide both  $L$  &  $C$  by same factor used to multiply  $f$  by  $k_f$

### Magnitude Scaling

- If components too little/large, scale up/down component values without changing  $f$

∴ Multiply all impedances by  $k_m$ : ( $\omega' = \omega$ )

$$\begin{aligned} Z_R' &= k_m Z_R = k_m R \\ R' &= k_m R \end{aligned}$$

$$\begin{aligned} Z_L' &= k_m Z_L = j\omega k_m L \\ L' &= k_m L \end{aligned}$$

$$\begin{aligned} Z_C' &= k_m Z_C = \frac{1}{j\omega C / k_m} \\ C' &= \frac{C}{k_m} \end{aligned}$$

### Magnitude & Frequency scaling

- Increase RLC by  $k_m$ , sh.f of response by  $k_f$ :

$$R' = k_m R, \quad L' = \frac{k_m}{k_f} L, \quad C' = \frac{1}{k_m k_f} C, \quad \omega' = k_f \omega$$