


Filters

February 8, 2020 6:45 PM

Definition

- Filters out unwanted signals
- want "brick wall" transfer characteristics
 $|Y(\omega)| = |H(\omega)| \cdot |X(\omega)|$


Ideal Low pass Filter

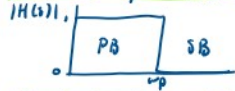


Ideal High pass Filter



Ideal Bandpass Filter

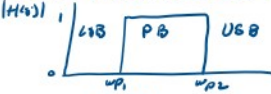


Ideal Stopband Filter

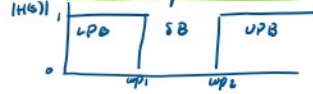

- ω_p = cut off f


Real Filter

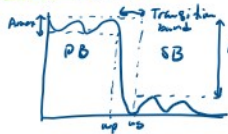

- A_{max} = max variation in passband
- ω_p, ω_s = selectivity function
- A_{min} = min attenuation

Filter classification

- How quickly they stop

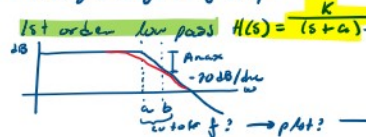

Roll @ cutoff f ω_c

HP Prime Plotting:

- no complex fts & linear axes
- fine $\omega \rightarrow$ fine 10^x $x \rightarrow$ decades

$$\text{ex. } H(s) = \frac{25000}{(s+6500)}, \quad \alpha = 20 \log_{10} \frac{25000}{\sqrt{\omega^2 + 6500^2}}$$

$$X = \log_{10} \omega \rightarrow \omega = 10^X, \quad X = \text{decades}$$

$$\alpha = 20 \log_{10} \frac{25000}{\sqrt{(10^X)^2 + 6500^2}}$$

- Approximate cutoff:

- pole on edge of BW = approx. cutoff f
- Actual cutoff f depends on A_{min}

Classification by construction

Passive: only RLC

Active: RLC + opamp

ex. Low pass



$$H(s) = \frac{1}{s^2 + 1}$$


High Pass



$$H(s) = \frac{s^2}{s^2 + 1}$$



$$H(s) = \frac{s}{s^2 + 1}$$

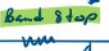

$$H(s) = \frac{s^2 + 1}{s^2 + 1}$$




Quality Factor

- For band pass, cutoff f ω_h & ω_l \rightarrow attenuation goes up by 20 dB, "Half Power f"

- "Center f" ω_0 \rightarrow mean of ω_h & ω_l

- Bandwidth $BW = \omega_h - \omega_l$

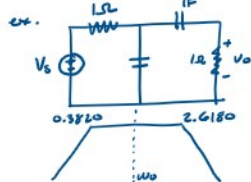- Filter selectivity measured by quality factor $Q = \frac{\omega_0}{BW}$



- Center f? BW ? Q ?

$$H(s) = \frac{3}{s^2 + 3s + 1} \rightarrow \text{Band Pass}$$

\rightarrow roots (1, 3, 1): poles = -0.3820, -2.6180

\rightarrow Geometric Mean: $\sqrt{x_1 x_2 \dots x_n}$

$$\omega_0 = \sqrt{0.3820 \cdot 2.6180} = 1 \text{ rad/s}$$


$$BW = 2.618 - 0.382 = 2.236$$

$$Q = \frac{\omega_0}{BW} = 0.447227$$

Sallen-Key (Active Filters)

- Replace resistors by impedances
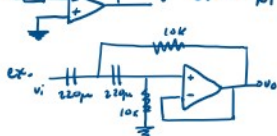
$$v_i \rightarrow v_o \quad G_v = -\frac{R_2}{R_1} \rightarrow H(s) = -\frac{Z_2(s)}{Z_1(s)}$$



$$H(s) = \frac{121s^2}{121s^2 + 11000s + 26000000}$$

Scaling & Recipes

- Filter "cookbooks"
- Scale filters for different components

Scaling & Recipes

- Filter "cookbooks"
- Scale filters for different components

Frequency Scaling

- Want same impedance Z but at k_f times original f
- need new values for L & C :
 $Z_L = j\omega L = j\omega k_f L' \rightarrow L' = \frac{L}{k_f}$
 $Z_C = \frac{1}{j\omega C} = \frac{1}{j\omega k_f C'} \rightarrow C' = \frac{C}{k_f}$
- Divide both L & C by same factor used to multiply f by k_f

Magnitude Scaling

- If components too little/too large, scale up/down component values without changing f
- Multiply all impedances by k_m : ($\omega' = \omega$)

$$\begin{aligned} Z_R' &= k_m Z_R = k_m R, & Z_L' &= k_m Z_L = j\omega k_m L, & Z_C' &= k_m Z_C = \frac{1}{j\omega k_m C} \\ R' &= k_m R, & L' &= k_m L, & C' &= \frac{C}{k_m} \end{aligned}$$

Magnitude & Frequency Scaling

- Increase R, L, C by k_m , shift f response by k_f :
 $R' = k_m R, \quad L' = \frac{k_m}{k_f} L, \quad C' = \frac{1}{k_m k_f} C, \quad \omega' = k_f \omega$

Webwork FLT

Homework

Sets

FLT

Problem 6

User Settings

Grades

Problems

Problem 1

Problem 2

Problem 3

Problem 4

Problem 5

Problem 6

Problem 7

Problem 8

Problem 9

FLT: Problem 6


Previous Problem

Problem List

Next Problem

(11 points)

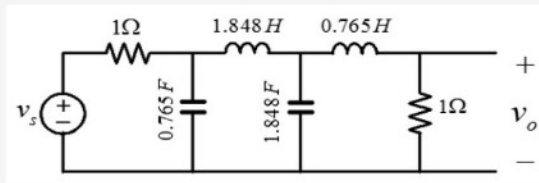A fourth-order Butterworth low pass filter is shown in the figure below. Using "scaling" replace the two resistors by 7 kilo ohm resistors and determine what must be the values of the inductor and the capacitor for a cutoff frequency of 12 kHz.



Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

$L_{left} =$ H

$C_{left} =$ F

$L_{right} =$ H

$C_{right} =$ F

$$\omega_0 = 12 \text{ kHz} = \frac{6000}{\pi}$$

Scaling \rightarrow (Filters Video)

$$R = 1 \Omega \rightarrow 7 \text{ k}\Omega$$

$$\omega = 12 \text{ kHz} \cdot 2\pi = 24 \text{ k rad/s}$$

Magnitude Scaling factor $k_m = 7 \text{ k}$

frequency scaling factor $k_f = 24 \text{ k rad/s}$

original f : $\omega_0 = 1 \text{ rad/s} \rightarrow$ needed to plot Bode plot
find cutoff f & type of filter...

$$\therefore \omega_0' = 24 \text{ k rad/s}$$

$$L_1' = \frac{k_m \cdot L}{k_f} = 0.171569 \text{ H}$$

$$C_1' = \frac{1}{k_m k_f} C = 1.4494468 \times 10^{-9} \text{ F}$$

$$L_2' = 7.102289 \times 10^{-2} \text{ H}$$

$$C_2' = 3.50140875 \times 10^{-9} \text{ F}$$

FLT: Problem 7


Previous Problem

Problem List

Next Problem

(11 points)

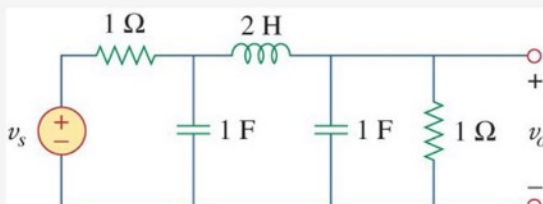You pick up a third order Butterworth filter from a "filters cookbook" and want to modify it so the capacitors are 25 nF and it has a cut off frequency of 3 kilo hertz. Determine the values of the inductor and the resistors.



Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

$R =$ Ω

$L =$ H

Scaling:

$$C = 1 \text{ F} \rightarrow 25 \text{ nF}$$

$$\omega_0 = 1 \rightarrow 3 \text{ kHz} \cdot 2\pi = 6 \text{ k rad/s}$$

(Find TF, Bode Plot)

$$\therefore k_f = 6 \text{ k rad/s}$$

$$C' = \frac{1}{k_m k_f} C$$

$$\therefore k_m = 2122.065908$$

$$R' = k_m R$$

$$\therefore R = 2122.06590789 \Omega$$

$$L' = \frac{k_m}{k_f} L$$

$$\therefore L = 0.22515818 \text{ H}$$

FLT: Problem 8

Sets

FLT

Scaling:

Sets

FLT

Problem
8

User Settings

Grades

Problems

Problem 1 ✓

Problem 2 ✓

Problem 3 ✓

Problem 4

Problem 5

Problem 6 ✓

Problem 7

Problem 8

Problem 9

FLT: Problem 8


Previous Problem

Problem List

Next Problem

(11 points)

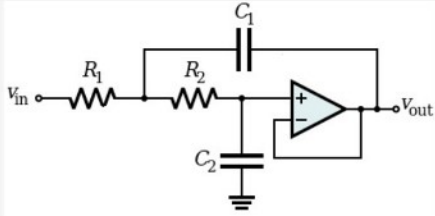A Sallen Key low pass filter in its canonical form is shown in the figure, with resistors of one ohm each and where the capacitor on the top is 1.4142 F and the capacitor on the bottom is 0.7071 F. If we want to use 16 kilo ohm resistors instead and we need it to have a cut off frequency of 21 kilo hertz, what should be the values for the two capacitors.



Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

$C_1 =$ F

$C_2 =$ F

Scaling:

$$R = 1\Omega \rightarrow 16k\Omega$$

$$\omega = 1 \rightarrow 21kHz \cdot 2\pi = 42000\text{ rad/s}$$

(Find ω initial: Find TF, draw Bode Plot)

$$\therefore k_m = 16k$$

$$k_f = 42000\text{ rad/s}$$

$$C' = \frac{1}{k_m k_f} C$$

$$\therefore C_1 = 6.69871787 \times 10^{-10} \text{ F}$$

$$C_2 = 3.34935893 \times 10^{-10} \text{ F}$$