


State Space

April 16, 2020 4:54 PM

State

- Status of system w/ state known at t_0 for CT

RLC circuit

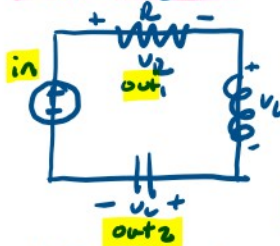

$$\dot{x}(t) = A x(t) + B u(t) \rightarrow \text{State diff eqn.}$$

$$y(t) = C x(t) + D u(t) \rightarrow \text{Output eqn.}$$

output u

Feedforward m

Inputs: $x_1 = v_C$

$x_2 = i$

Outputs: $y_1 = v_C = x_1$

$y_2 = R i = R x_2$

V. input: $u_1 =$

$$\text{KVL: } V = iR + v_L + v_C$$

$$V = iR + L \frac{di}{dt} + v_C$$

$$\frac{di}{dt} = \frac{1}{L} V - \frac{R}{L} i - \frac{1}{L} v_C$$

$$\therefore \begin{aligned} \dot{x}_2 &= \frac{1}{L} u - \frac{R}{L} x_2 - \frac{1}{L} x_1 \\ \dot{x}_1 &= \frac{1}{C} x_2 \end{aligned}$$

$$\frac{dv_C}{dt} = \frac{1}{C} i$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1/L \\ -1/L & -R/L \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} u$$

$$\begin{bmatrix} y_1 \\ y_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & R \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} u$$