

## 2nd Order Circuits

### Laplace domain:


#### Inductor:

$$v(t) = L \frac{di(t)}{dt} \rightarrow V(s) = sLI(s) - Li(0^-)$$
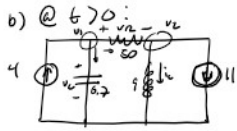
#### Capacitor:

$$\int i(t) dt \rightarrow \frac{I(s)}{s} + \frac{1}{s} \int_{-\infty}^0 i(t) dt$$


$$v(t) = \frac{1}{C} \int i(t) dt \rightarrow V(s) = \frac{I(s)}{sC} + \frac{v(0^-)}{s}$$



KVL:  $4 = i_C + i_R$   
 $4 = C \frac{dv_C}{dt} + \frac{v_C}{R}$   
 $\frac{dv_C(0^+)}{dt} = \frac{4}{0.7} = 5.71429 \text{ V/s}$

KVL:  $L \frac{di_L}{dt} = v_L - v_C$   
 $\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{4}{9} = 0.44 \text{ A/s}$

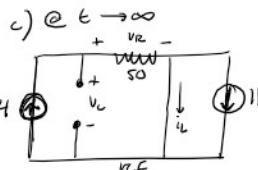KCL:  $Ri_R = v_R$   
 $v_R(0^+) = 0 \text{ V/s}$



$v_C(\infty) = 4 \cdot 50 = 200 \text{ V}$   
 $v_L(\infty) = v_R(\infty) = 100 \text{ V}$   
 $i_L(\infty) = 4 - 11 = -7 \text{ A}$

#### Capacitor

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_{-\infty}^t i dt$$

$$v(0^+) = v(0^-)$$

#### Inductor

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{-\infty}^t v dt$$

$$i(0^+) = i(0^-)$$


(8 points)

For the circuit shown below, let  $I = 4u(t) \text{ A}$ ,  $C = 0.7 \text{ F}$ ,  $R = 50 \Omega$ ,  $L = 9 \text{ H}$  and  $I_1 = 11 \text{ A}$ . Find:

(a)  $i_L(0^+)$ ,  $v_C(0^+)$ ,  $v_R(0^+)$

(b)  $\frac{di_L(0^+)}{dt}$ ,  $\frac{dv_C(0^+)}{dt}$ ,  $\frac{dv_R(0^+)}{dt}$

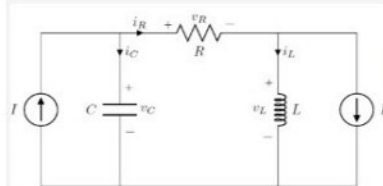(c)  $i_L(\infty)$ ,  $v_C(\infty)$ ,  $v_R(\infty)$



Note: In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

$i_L(0^+)$	A	$\frac{di_L(0^+)}{dt}$	A/s	$i_L(\infty)$	A
$v_C(0^+)$	V	$\frac{dv_C(0^+)}{dt}$	V/s	$v_C(\infty)$	V
$v_R(0^+)$	V	$\frac{dv_R(0^+)}{dt}$	V/s	$v_R(\infty)$	V

$S: 1 \rightarrow n = \frac{1}{5}$

①  $\frac{V_2}{V_1} = \frac{1}{5}$

②  $\frac{I_2}{I_1} = 5$

KCL: ③  $I_2 = \frac{V_1 - V_3}{\frac{1}{5 \times 10^{-3}}} + I_1$


④  $V_4 = V_1 - V_2$   
 $\frac{V_3 - V_4}{50 \times 10^{-3} S} = I_2 + \frac{V_4 + 200 \angle 0^\circ}{20}$

⑤  $\frac{V_3 - V_4}{50 \times 10^{-3} S} = I_2 + \frac{V_3 - V_4}{50 \times 10^{-3} S}$   
 $\frac{V_1 - V_3}{\frac{1}{5 \times 10^{-3}}} = \frac{V_3}{55} + \frac{V_3 - V_4}{50 \times 10^{-3} S}$

$\rightarrow S = 21j$

$\rightarrow \text{solve: } V_1 = 1833.5 \angle -3.13656 \text{ rad}$

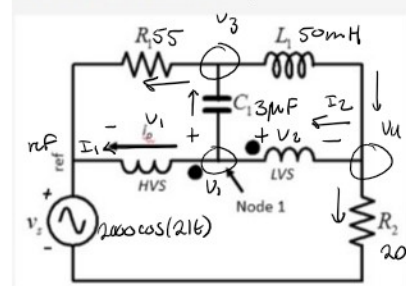An ideal transformer circuit.  $i_1 = 5.80227 \angle -1.4897 \text{ rad}$



Report the peak value of  $V_1$   V

Report the phase of  $V_1$ :  rad

Report the peak value of  $I_1$ :  mA

report the phase of  $I_1$ :  rad

$n = \frac{3}{1} = 3$

①  $\frac{V_2}{V_1} = 3 \therefore V_1, V_2 \rightarrow \text{diff. polarities}$

②  $\frac{I_2}{I_1} = \frac{1}{3} \therefore I_1, I_2 \rightarrow \text{same direction}$

KCL: ③  $\frac{45 \angle 0^\circ - V_1}{65} = I_1 + \frac{V_1 - V_2}{\frac{1}{6 \times 10^{-3} S}}$


④  $\frac{V_1 - V_2}{\frac{1}{6 \times 10^{-3} S}} = I_2 + \frac{V_2}{55}$

$\rightarrow S = 7j$

$\rightarrow \text{solve: } i_2 = 0.35307 \cos(7t + 0.260354)$

## Transformer

### Dot Convention

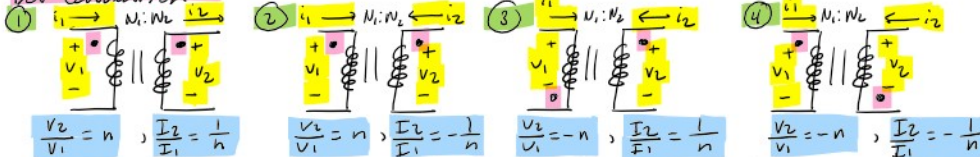

- If current enters dotted terminal, opposite dotted terminal = (+)  
 -  $V_1, V_2$  act as sources

$\rightarrow$  2nd coil induces mutual inductance on 1st coil

### Coils in Series

$+ V_{1M} + + V_{2M} =$

$+ V_1 + + V_2 =$

$+ V_1 + + V_2 =$

Voltage Drop:  $V = V_1 + V_2 + V_{1M} + V_{2M}$

Total Inductance:  $L = L_1 + L_2 + 2M$

$- V_{1M} + - V_{2M} =$

$- V_1 + - V_2 =$

$- V_1 + - V_2 =$




Voltage Drop:  $V = V_1 + V_2 - V_{1M} - V_{2M}$

Total Inductance:  $L = L_1 + L_2 - 2M$

$n = \frac{N_2}{N_1}$

-  $V_1, V_2$  depends on current directions  
 -  $V_{1M}, V_{2M}$  depends on windings of both coils

## Equivalent Networks

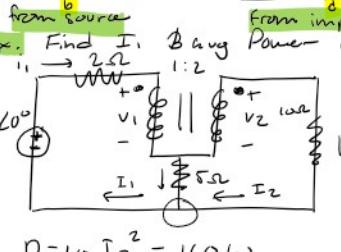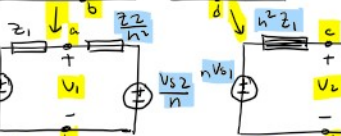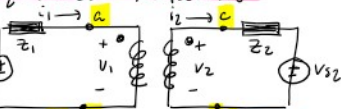

$n = \frac{2}{1} = 2$

KCL: ③  $\frac{46 \angle 0^\circ - 2I_1 - V_1}{5} + I_2 = I_1$

④  $\frac{46 \angle 0^\circ - 2I_1 - V_1 + V_2}{10} = I_2$

$\rightarrow \text{solve: } V_1 = 10 \text{ V}, V_2 = 20 \text{ V}$


$$P = 10 I_2^2 = 160 \text{ W}$$

$$\text{Solve: } V_1 = 10 \text{ V}, V_2 = 20 \text{ V}$$

$$I_1 = 8 \text{ A}, I_2 = 4 \text{ A}$$

### 3 Phase circuits

#### Balanced Y-Y Connection

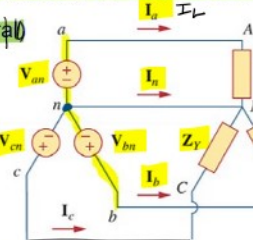

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}| = \sqrt{3} V_p$$

$$I_a + I_b + I_c = 0$$

$$I_n = -(I_a + I_b + I_c) = 0$$

$$V_n = Z_n \cdot I_n = 0$$

#### Power

##### Instantaneous Power

$$p(t) = p_a(t) + p_b(t) + p_c(t) = 3 V_p I_p \cos(\theta)$$


##### Phase Power

$$\text{Avg Power: } P_p = V_p I_p \cos \theta$$

$$\text{Reactive Power: } Q_p = V_p I_p \sin \theta$$

$$\text{Apparent Power: } S_p = V_p I_p$$
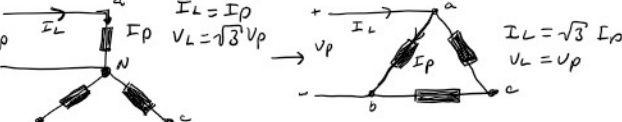
$$\text{Complex Power: } S_p = V_p \cdot I_p^* = P_p + j Q_p = V_p I_p \angle \theta$$



#### Total Power

$$\text{Avg Power: } P = 3 P_p = 3 V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$\text{Reactive Power: } Q = 3 Q_p = 3 V_p I_p \sin \theta = \sqrt{3} V_L I_L \sin \theta$$

$$\text{Apparent Power: } |S| = 3 V_p I_p = \sqrt{3} V_L I_L$$

$$\text{Complex Power: } S = 3 S_p = 3 V_p I_p^* = P + j Q = 3 V_p I_p \angle \theta = \sqrt{3} V_L I_L \angle \theta$$

#### Y-Y

$$V_{ab} = V_{an} - V_{bn} = 160 \angle 0^\circ - 160 \angle -120^\circ = 277.12813 \angle 30^\circ \text{ V}$$

$$I_a = \frac{V_{ab}}{Z_f + Z_L} = \frac{160 \angle 0^\circ}{35 + j6 + 0.4 + j0.7} = 4.4409335 \angle -10.71734^\circ \text{ A}$$

$$I_p = I_L = 4.4409335 \angle -10.71734^\circ \text{ A}$$

$$S_s = 3 V_p \cdot I_p^* = 3(160 \angle 0^\circ) \cdot (4.4409335 \angle -10.71734^\circ)^* = 2131.65 \angle 10.7173^\circ \text{ VA}$$

$$S_L = 3 |I_L|^2 \cdot Z_L = 4.7200889 \angle 60.2551^\circ \text{ VA}$$

#### Y-Δ

$$V_{ab} = V_{an} - V_{bn} = 277.12813 \angle 30^\circ \text{ V}$$

$$I_a = \frac{V_{ab}}{Z_f + Z_\Delta} = \frac{160 \angle 0^\circ}{35 + j6 + 0.1333 + j0.2333} = 4.48405 \angle -10.0606^\circ$$

$$I_p = \frac{V_{ab}/3}{Z_f + Z_Y} = \frac{277.12813 \angle 30^\circ}{35 + j6 + 0.1333 + j0.2333} = 2.5888 \angle 19.939^\circ$$

$$S_s = 2131.64 \angle 10.0606^\circ$$

$$S_L = 3 \cdot |I_L|^2 \cdot Z_\Delta = 314.48405 \angle -10.0606^\circ (0.4 + j0.7)$$

$$= 16.2678 \angle 60.257^\circ \text{ VA}$$

#### Δ-Δ

$$V_L = V_p = 160 \angle 0^\circ$$

$$I_L = \frac{V_{ab}}{Z_f + Z_\Delta} = \frac{92.37604 \angle -30^\circ}{35 + j6 + 0.4 + j0.7} = 2.5639 \angle -40.7173^\circ$$

$$I_p = \frac{V_{ab}/3}{Z_f + Z_Y} = \frac{160 \angle 0^\circ / 3}{35 + j6 + 0.1333 + j0.2333} = 1.4445 \angle -10.0606^\circ$$

$$S_s = 717.36 \angle 10.0606^\circ$$

$$S_p = 5.4026 \angle 60.257^\circ$$


#### Δ-Y

$$V_L = V_p = 160 \angle 0^\circ$$


$$I_a = \frac{V_{ab}}{Z_f + Z_Y} = \frac{92.37604 \angle -30^\circ}{35 + j6 + 0.4 + j0.7} = 2.5639 \angle -40.7173^\circ$$

$$I_p = I_L = 2.5639 \angle -40.7173^\circ \text{ A}$$



#### Balanced Y-Δ Connection

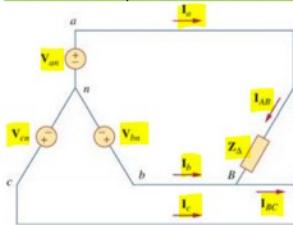

#### Convert Δ → Y

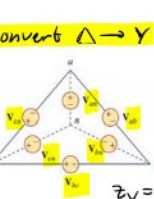
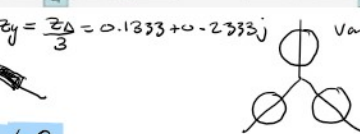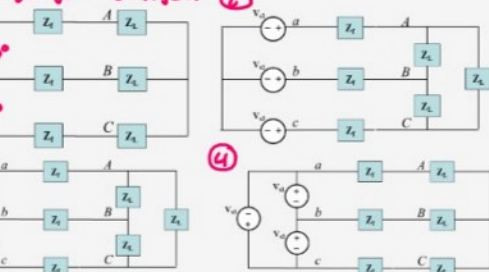
$$Z_Y = \frac{Z_\Delta}{3}, Z_\Delta = 3 Z_Y$$



#### AC Power

$$\text{Complex Power: } S = P + j Q = V_{rms} \cdot I_{rms}^* = V_{rms} I_{rms} \angle (\theta_v - \theta_i)$$

$$\text{Apparent Power: } |S| = V_{rms} I_{rms} = \sqrt{P^2 + Q^2}$$

$$\text{Real Power: } P = \text{Re}(S) = S \cos(\theta_v - \theta_i)$$

$$\text{Reactive Power: } Q = \text{Im}(S) = S \sin(\theta_v - \theta_i)$$


$$\text{Power Factor: } P/S = \cos(\theta_v - \theta_i)$$

$$\text{Power Factor Correction: Total Reactive Power: } Q_1 + Q_2 = 1.8 \text{ kVAR}$$

$$\text{- Add capacitor in parallel: } Q_c = -(Q_1 + Q_2) = -1.8 \text{ kVAR}$$

$$\text{- Complex Power received by capacitor: } S_c = -j \omega |V|^2 = j Q_c$$

$$3^\circ \text{ A} \rightarrow C = \frac{Q_c}{\omega |V|^2} = \frac{1.8 \times 10^3}{2\pi \cdot 60 \cdot 120^2} = 331.6 \mu\text{F}$$

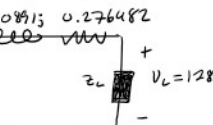

$$V_s \angle \theta_s = V_L \angle \theta_{VL} + V_C \angle \theta_{VC} = I_{rms} \cdot Z_L + 128 \angle \theta_{VL}$$

$$128 \angle \theta_s = (28)(0.276482 + j1.10891j) + 128 \angle \theta_{VL}$$

$$V_s \angle \theta_s = V_s \cos(\theta_s) + j V_s \sin(\theta_s)$$

$$128 \cos(\theta_s) + j 128 \sin(\theta_s) = 7.741496 + j 31.04448 + 128 \cos(\theta_{VL}) + j 128 \sin(\theta_{VL})$$

$$\text{Re(): } 128 \cos(\theta_s) = 7.741496 + 128 \cos(\theta_{VL})$$

$$\text{Im(): } 128 \sin(\theta_s) = 31.04448 + 128 \sin(\theta_{VL})$$

$$\rightarrow \text{solve: } \theta_s = -6.8192254^\circ \rightarrow \text{pf angle @ source}$$

$$\theta_{VL} = -21.1807438^\circ$$

$$|S| = V_{rms} \cdot I_{rms} = (128)(28) = 3584 \text{ VA}$$

$$P = \text{Re}(S) = |S| \cos(\theta_v - \theta_i) = 3584 \cos(-6.8192254^\circ) = 3558.645788 \text{ W}$$

$$Q = \text{Im}(S) = |S| \sin(\theta_v - \theta_i) = 3584 \sin(-6.8192254^\circ) = -425.553976 \text{ VAR}$$

$$P = \text{Re}(S) = |S| \cos(\theta_v - \theta_i) = 3584 \cos(-21.1807438^\circ) = 3341.8839 \text{ W}$$



$V_L = V_P = 160 \angle 0^\circ$   
 $I_A = \frac{V_{AB}}{Z_f + Z_y} = \frac{92.3604 \angle -30^\circ}{35 + 6j + 0.4 + 0.7j} = 2.5639 \angle -40.717^\circ$   
 $I_P = I_L = 2.5639 \angle -40.717^\circ$   
 $S_S = 717.36 \angle 10.717^\circ$   
 $S_L = 16.2078 \angle 60.257^\circ$


## AC circuits

### Superposition

- Multiple frequencies involved: solve phasor circuit
- Sum of time-domain responses
- Short V sources Open current source

## Connecting 2-Port Networks


### Cascade

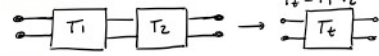

### Series




### Parallel

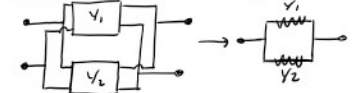

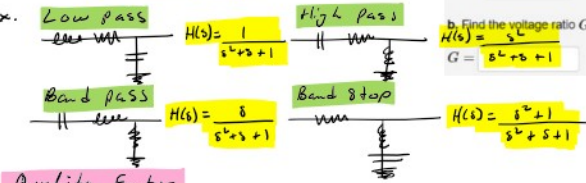
## Classification by construction

- Passive: only RLC
- Active: RLC + opamp



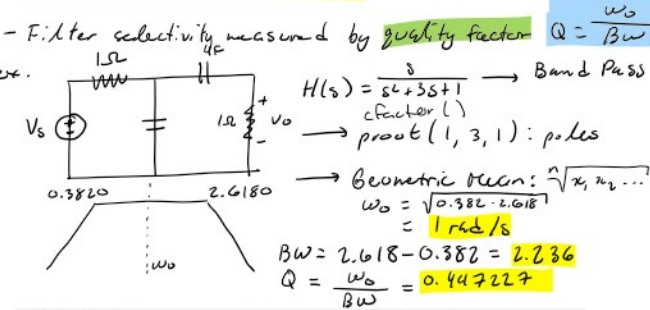
## Quality Factor

- For band pass, cutoff f  $\omega_h$  &  $\omega_L$
- "Center f"  $\omega_0 \rightarrow$  mean of  $\omega_h$  &  $\omega_L$
- Bandwidth  $BW = \omega_h - \omega_L$
- Filter selectivity measured by quality factor  $Q = \frac{\omega_0}{BW}$



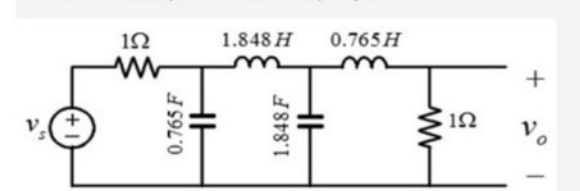A fourth-order Butterworth low pass filter is shown in the figure below. Using "scaling" replace the two resistors by 7 kilo ohm resistors and determine what must be the value of the inductor and the capacitor for a cutoff frequency of 12 kHz.



$\omega_0 = 12 \text{ kHz} = \frac{6000}{\pi}$

Scaling  $\rightarrow$  (Filters Video)

$R = 1\Omega \rightarrow 7k\Omega$


Magnitude Scaling factor

$k_m = 7k$

Frequency scaling factor

b)  $|S| = V_{rms} \cdot I_{rms} = (128)(78) = 3584 \text{ VA}$   
 $P = \text{Re}(S) = |S| \cos(\theta_v - \theta_i) = 3584 \cos(-6.8192254^\circ) = 3558.645788 \text{ W}$   
 $Q = \text{Im}(S) = |S| \sin(\theta_v - \theta_i) = 3584 \sin(-6.8192254^\circ) = -425.553376 \text{ VAR}$   
 $P = \text{Re}(S) = |S| \cos(\theta_v - \theta_i) = 3584 \cos(-21.1867438^\circ) = 3341.8839 \text{ W}$   
 $Q = \text{Im}(S) = |S| \sin(\theta_v - \theta_i) = 3584 \sin(-21.1867438^\circ) = -1294.4393783 \text{ VAR}$

### 1A/2A Test Source

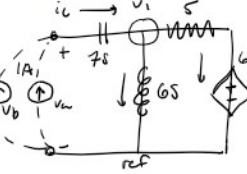

### 1A Source

KCL:  $1 = \frac{V_1}{6S} + \frac{V_1 - 6(1)}{S}$

$V_A = V_1 + (1)7S$

$V_A = 10.5424 + 0.44633j$

$V_B = V_1 + 2 \cdot 7S$

$V_B = 21.084858 + 0.892678j$

$V_C = V_1 + 2 \cdot 7S$

$V_C = 21.084858 + 0.892678j$

$V_D = V_1 + 2 \cdot 7S$

$V_D = 21.084858 + 0.892678j$

$V_E = V_1 + 2 \cdot 7S$

$V_E = 21.084858 + 0.892678j$

$V_F = V_1 + 2 \cdot 7S$

$V_F = 21.084858 + 0.892678j$

$V_G = V_1 + 2 \cdot 7S$

$V_G = 21.084858 + 0.892678j$

$V_H = V_1 + 2 \cdot 7S$

$V_H = 21.084858 + 0.892678j$

$V_I = V_1 + 2 \cdot 7S$

$V_I = 21.084858 + 0.892678j$

$V_J = V_1 + 2 \cdot 7S$

$V_J = 21.084858 + 0.892678j$

$V_K = V_1 + 2 \cdot 7S$

$V_K = 21.084858 + 0.892678j$

$V_L = V_1 + 2 \cdot 7S$

$V_L = 21.084858 + 0.892678j$

$V_M = V_1 + 2 \cdot 7S$

$V_M = 21.084858 + 0.892678j$

$V_N = V_1 + 2 \cdot 7S$

$V_N = 21.084858 + 0.892678j$

$V_O = V_1 + 2 \cdot 7S$

$V_O = 21.084858 + 0.892678j$

$V_P = V_1 + 2 \cdot 7S$

$V_P = 21.084858 + 0.892678j$

$V_Q = V_1 + 2 \cdot 7S$

$V_Q = 21.084858 + 0.892678j$

$V_R = V_1 + 2 \cdot 7S$

$V_R = 21.084858 + 0.892678j$

$V_S = V_1 + 2 \cdot 7S$

$V_S = 21.084858 + 0.892678j$

$V_T = V_1 + 2 \cdot 7S$

$V_T = 21.084858 + 0.892678j$

$V_U = V_1 + 2 \cdot 7S$

$V_U = 21.084858 + 0.892678j$

$V_V = V_1 + 2 \cdot 7S$

$V_V = 21.084858 + 0.892678j$

$V_W = V_1 + 2 \cdot 7S$

$V_W = 21.084858 + 0.892678j$

$V_X = V_1 + 2 \cdot 7S$

$V_X = 21.084858 + 0.892678j$

$V_Y = V_1 + 2 \cdot 7S$

$V_Y = 21.084858 + 0.892678j$

$V_Z = V_1 + 2 \cdot 7S$

$V_Z = 21.084858 + 0.892678j$

$V_{AA} = V_1 + 2 \cdot 7S$

$V_{AA} = 21.084858 + 0.892678j$

$V_{AB} = V_1 + 2 \cdot 7S$

$V_{AB} = 21.084858 + 0.892678j$

$V_{AC} = V_1 + 2 \cdot 7S$

$V_{AC} = 21.084858 + 0.892678j$

$V_{AD} = V_1 + 2 \cdot 7S$

$V_{AD} = 21.084858 + 0.892678j$

$V_{AE} = V_1 + 2 \cdot 7S$

$V_{AE} = 21.084858 + 0.892678j$

$V_{AF} = V_1 + 2 \cdot 7S$

$V_{AF} = 21.084858 + 0.892678j$

$V_{AG} = V_1 + 2 \cdot 7S$

$V_{AG} = 21.084858 + 0.892678j$

$V_{AH} = V_1 + 2 \cdot 7S$

$V_{AH} = 21.084858 + 0.892678j$

$V_{AI} = V_1 + 2 \cdot 7S$

$V_{AI} = 21.084858 + 0.892678j$

$V_{AJ} = V_1 + 2 \cdot 7S$

$V_{AJ} = 21.084858 + 0.892678j$

$V_{AK} = V_1 + 2 \cdot 7S$

$V_{AK} = 21.084858 + 0.892678j$

$V_{AL} = V_1 + 2 \cdot 7S$

$V_{AL} = 21.084858 + 0.892678j$

$V_{AM} = V_1 + 2 \cdot 7S$

$V_{AM} = 21.084858 + 0.892678j$

$V_{AN} = V_1 + 2 \cdot 7S$

$V_{AN} = 21.084858 + 0.892678j$

$V_{AO} = V_1 + 2 \cdot 7S$

$V_{AO} = 21.084858 + 0.892678j$

$V_{AP} = V_1 + 2 \cdot 7S$

$V_{AP} = 21.084858 + 0.892678j$

$V_{AQ} = V_1 + 2 \cdot 7S$

$V_{AQ} = 21.084858 + 0.892678j$

$V_{AR} = V_1 + 2 \cdot 7S$

$V_{AR} = 21.084858 + 0.892678j$

$V_{AS} = V_1 + 2 \cdot 7S$

$V_{AS} = 21.084858 + 0.892678j$

$V_{AT} = V_1 + 2 \cdot 7S$

$V_{AT} = 21.084858 + 0.892678j$

$V_{AU} = V_1 + 2 \cdot 7S$

$V_{AU} = 21.084858 + 0.892678j$

$V_{AV} = V_1 + 2 \cdot 7S$

$V_{AV} = 21.084858 + 0.892678j$

$V_{AW} = V_1 + 2 \cdot 7S$

$V_{AW} = 21.084858 + 0.892678j$

$V_{AX} = V_1 + 2 \cdot 7S$

$V_{AX} = 21.084858 + 0.892678j$

$V_{AY} = V_1 + 2 \cdot 7S$

$V_{AY} = 21.084858 + 0.892678j$

$V_{AZ} = V_1 + 2 \cdot 7S$

$V_{AZ} = 21.084858 + 0.892678j$

$V_{BA} = V_1 + 2 \cdot 7S$

$V_{BA} = 21.084858 + 0.892678j$

$V_{BB} = V_1 + 2 \cdot 7S$

$V_{BB} = 21.084858 + 0.892678j$

$V_{BC} = V_1 + 2 \cdot 7S$

$V_{BC} = 21.084858 + 0.892678j$

$V_{BD} = V_1 + 2 \cdot 7S$

$V_{BD} = 21.084858 + 0.892678j$

$V_{BE} = V_1 + 2 \cdot 7S$

$V_{BE} = 21.084858 + 0.892678j$

$V_{BF} = V_1 + 2 \cdot 7S$

$V_{BF} = 21.084858 + 0.892678j$

$V_{BG} = V_1 + 2 \cdot 7S$

$V_{BG} = 21.084858 + 0.892678j$

$V_{BH} = V_1 + 2 \cdot 7S$

$V_{BH} = 21.084858 + 0.892678j$

$V_{BI} = V_1 + 2 \cdot 7S$

$V_{BI} = 21.084858 + 0.892678j$

$V_{BJ} = V_1 + 2 \cdot 7S$

$V_{BJ} = 21.084858 + 0.892678j$

$V_{BK} = V_1 + 2 \cdot 7S$

$V_{BK} = 21.084858 + 0.892678j$

$V_{BL} = V_1 + 2 \cdot 7S$

$V_{BL} = 21.084858 + 0.892678j$

$V_{BM} = V_1 + 2 \cdot 7S$

$V_{BM} = 21.084858 + 0.892678j$

$V_{BN} = V_1 + 2 \cdot 7S$

$V_{BN} = 21.084858 + 0.892678j$

$V_{BO} = V_1 + 2 \cdot 7S$

$V_{BO} = 21.084858 + 0.892678j$

$V_{BP} = V_1 + 2 \cdot 7S$

$V_{BP} = 21.084858 + 0.892678j$

$V_{BQ} = V_1 + 2 \cdot 7S$

$V_{BQ} = 21.084858 + 0.892678j$

$V_{BR} = V_1 + 2 \cdot 7S$

$V_{BR} = 21.084858 + 0.892678j$

$V_{BS} = V_1 + 2 \cdot 7S$

$V_{BS} = 21.084858 + 0.892678j$

$V_{BT} = V_1 + 2 \cdot 7S$

$V_{BT} = 21.084858 + 0.892678j$

$V_{BU} = V_1 + 2 \cdot 7S$

$V_{BU} = 21.084858 + 0.892678j$

$V_{BV} = V_1 + 2 \cdot 7S$

$V_{BV} = 21.084858 + 0.892678j$

$V_{BW} = V_1 + 2 \cdot 7S$

$V_{BW} = 21.084858 + 0.892678j$

$V_{BX} = V_1 + 2 \cdot 7S$

$V_{BX} = 21.0848$

Scaling → (Filters Video)

$R = 1\Omega \rightarrow 2k\Omega$

$\omega = 12k\text{Hz} \cdot 2\pi = 24k\text{ rad/s}$

$\omega_0 = 24k\text{ rad/s}$

$L' = \frac{k_m \cdot L}{k_f} = 0.1715694$

$C'_1 = \frac{1}{k_m k_f} C = 1.4494468 \times 10^{-9} \text{ F}$

$L'_2 = 7.102289 \times 10^{-2} \text{ H}$

$C'_2 = 3.50140875 \times 10^{-9} \text{ F}$

Magnitude Scaling factor

$k_m = 2k$

Frequency scaling factor

$k_f = 24k\text{ rad/s}$

original  $f$ :  $\omega_0 = 1\text{ rad/s}$

without changing  $f$


Multiply all impedances by  $k_m$ : ( $\omega' = \omega$ )  
 $Z_R = k_m Z_R = k_m R$ ,  $Z_L = k_m Z_L = j\omega k_m L$ ,  $Z_C = k_m Z_C = \frac{1}{j\omega k_m C}$   
 $R' = k_m R$ ,  $L' = k_m L$ ,  $C' = \frac{C}{k_m}$

Magnitude & frequency scaling

increase RLC by  $k_m$ , shift  $f$  response by  $k_f$ :

$R' = k_m R$ ,  $L' = \frac{k_m \cdot L}{k_f}$ ,  $C' = \frac{1}{k_m k_f} \cdot C$ ,  $\omega' = k_f \omega$

## Bode Plots

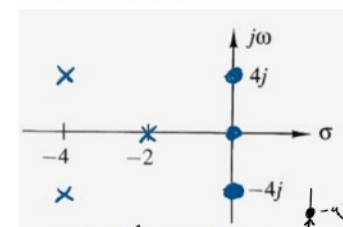

Complex Roots

$s^2 + 2s + 4 = 0$

$(s-4j)(s+4j): \omega_0 = \sqrt{0^2 + 4^2} = 4$   $\phi = \cos \theta = \frac{\omega_0}{\omega}$

$\therefore (s^2 + 2 \cdot 1 \cdot 4 + 4^2)$

$(s+4+4j)(s+4-4j): \omega_0 = \sqrt{4^2 + 4^2} = \sqrt{32}$   $\phi = \cos \theta = \frac{4}{\omega_0}$

$\therefore (s^2 + 2 \cdot 0.7071 \cdot \sqrt{32} + \sqrt{32}^2)$

$H(s) = \frac{9s(s-4j)(s+4j)}{(s+2)(s+4+4j)(s+4-4j)} = \frac{9s(s^2 + 2 \cdot 1 \cdot 4 + 4^2)}{(s+2)(s^2 + 2 \cdot 0.7071 \cdot \sqrt{32} + \sqrt{32}^2)}$   
 zeros: 0, 4 (double)  
 poles: 2, 5.65685 (double)

Starting PE:  $20 \log \left( \frac{4 \cdot (1) \cdot (4)^2}{(1)(5.65685)^2} \right) = 7.0436$

dB Error:  $\delta = 2j$


solve  $20 \log(H(s)) = 7.487841$   
 dB Error = |plot value - exact value|  
 =  $13.0643 - 7.487841$   
 =  $5.57645$

Phase Error:  $\delta = 2j$


solve  $\arg(H(s))$   
 phase Error = |plot value - exact value|  
 =  $12.4724 - 15.25512$   
 =  $2.78269$

Amplitude Plot: 2, 4, 5.65685

Slopes: 20, 40, -40

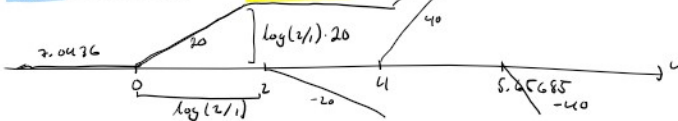


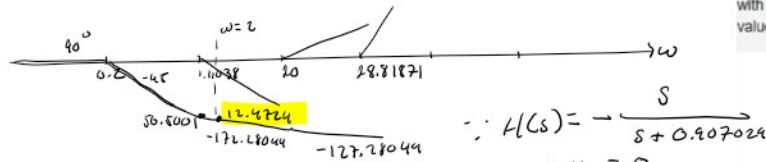Phase Plot: For complex roots:  $\omega_0/10^\circ$ ,  $\omega_0 \cdot 10^\circ$   
 0.2, 0.4, 1.11538, 2.0, 28.81871, 40  
 slopes: -45, 90, 45, 90, -90  
 $\infty$  -127.28044 127.28044  $-\infty$



$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{4.81s}{25137.1s^2 + 4.81s + 3900}$

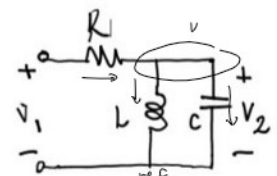with the circuit in the figure below. Determine and report the value of the capacitor, and the inductor.



$V_{in} = V_{out}$ ;  $H(s)$ ,  $V_1 = 1$ ,  $H(s) = V_2$

KCL:  $\frac{1 - V_2}{R} = \frac{V_2}{Ls} + \frac{V_2}{Cs}$

→ solve for  $V_2$ :


$V_2 = -\frac{1}{\frac{R}{Ls} - 1 - \frac{R}{Cs}} = \frac{-1}{-rCs - 1 - \frac{r}{Ls}} = \frac{-1}{\frac{-rCs^2 - Ls - r}{Ls}} \rightarrow \text{compare w/ } H(s):$   
 $Ls = 4.81s$

## Transfer Functions

Realize the transfer function (where  $a = 0.907029$ )

$H(s) = \frac{V_{out}}{V_{in}} = -\frac{s}{s+a}$

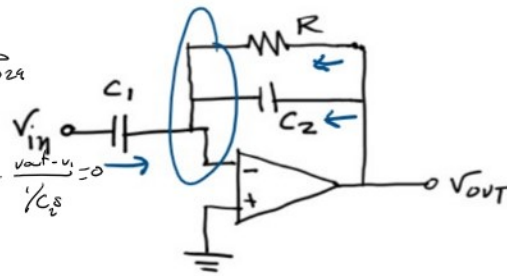with the circuit in the figure below. If the resistor is  $R = 4500 \Omega$ , determine and value of the two capacitors.



$H(s) = -\frac{s}{s+0.907029}$   
 NF;  $V_1 = 0$

KCL:  $\frac{1 - V_1}{C_1 s} + \frac{V_{out} - V_1}{4500} + \frac{V_{out} - V_1}{C_2 s} = 0$

→ solve for  $V_{out}$ :

$V_{out} = -\frac{4500 \cdot C_1 \cdot s}{4500 \cdot C_2 \cdot s + 1} = -\frac{4081.6305 C_1 \cdot s}{4081.6305 C_2 \cdot s + 0.907029}$

$V_{out} = -\frac{s}{s+0.907029}$

$\therefore C_1 = \frac{1}{4081.6305} \text{ F}$   $C_2 = \frac{1}{4081.6305} \text{ F}$

→ solve for  $v_1$ :

$$v_1 = -\frac{1}{-\frac{r}{ls} - 1 - \frac{r}{ls}} = \frac{-1}{-r ls - 1 - \frac{r}{ls}} = \frac{-1}{-\frac{r ls^2}{ls} - \frac{ls}{ls} - \frac{r}{ls}}$$

$$= \frac{-1}{-\frac{r ls^2 + ls + r}{ls}} = \frac{-ls}{-r ls^2 - ls - r} = \frac{ls}{r ls^2 + ls + r}$$

→ compare w/  $H(s)$ :

$$\frac{ls}{r ls^2 + ls + r} = \frac{4.81s}{25137.1s^2 + 4.81s + 3900}$$

$$\therefore l = 4.81$$

$$r = 3900$$

$$c = \frac{25137.1}{r \cdot l} = 1.34$$