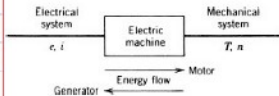


4. DC Machines


Tuesday, October 27, 2020 3:44 AM

4.1 Electromagnetic Conversion

1. Conductor moves in magnetic field, voltage induced in conductor
2. Conductor placed in magnetic field, conductor experiences mech. force
 → occur simultaneously when energy converted
 → **Motoring:** conductors in B-field, force produced on each conductor
 conductors on rotating structure @ speed
 voltage induced in each conductor
 → **Generating:** rotating structure driven by power (torque input)
 voltage induced in conductors rotating
 load connected to conductors, current delivers power to load
 & interact w/ B-field → Reaction torque opposes applied torque



- Power through mechanical shaft:

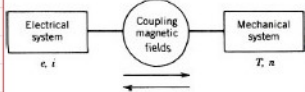


- Mech power on shaft: $P_m = T_m \cdot \omega_r$

Motoring & Generating Power

- flux & Armature current produce torque

Power Flow

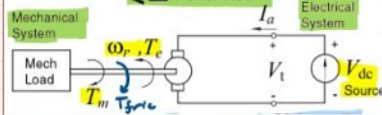


- Mechanical load torque T_m applied opposite to rotation ω_r (Generating)

$$T_e = T_{fric} + T_m$$

$$P_{out} = \omega_r T_m = P_m$$

$$P_{in} = V_t I_a$$

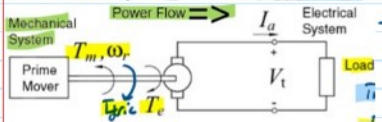

- Mechanical torque T_m applied in direction of rotation ω_r (Motoring)

$$T_m = T_{fric} + T_e$$

$$P_{in} = \omega_r T_m$$

$$P_{out} = V_t I_a$$

Motional Voltage e

- Voltage induced in conductor moving in magnetic field

- Faraday's Law: $e = \frac{d\phi}{dt}$ (V induced emf)


- conductor length l moves at speed v in field B : $e = Blv$

Electromagnetic Force &

- conductor moves in magnetic field

- Lorentz Force: $f = B l i_a$ (Mechanical force)

Force & Torque

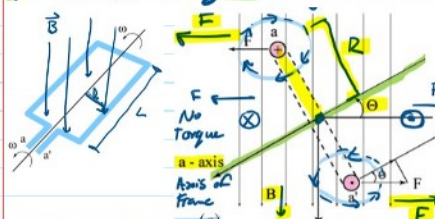

- Lorentz Force: $F = l B i_a \perp A$ loop

$$T_e = 2 R l B i_a \cos \theta$$

$$= A B i_a \cos \theta = \phi i_a \cos \theta$$

- Max Torque @ a -axis $\perp B$ & $T_e \sim \phi_p i_a$

Induced Voltage

$$\phi = B A \sin \theta = B 2 R l \sin \theta$$

→ rotate frame @ speed ω : $\theta = \omega t$

$$\phi = B A \sin(\omega t) = \phi_p \sin(\omega t) \rightarrow \phi_p = \text{peak flux}$$

$$\text{Faraday's law: } e = \frac{d\phi}{dt} = \omega \phi_p \cos(\omega t) \therefore e \sim \omega \phi_p$$

4.2 DC Machines


- operate as either generator / motor

Construction




- Armature winding placed on rotor
- Field winding placed on stator

Construction

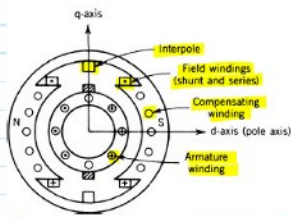

- Armature winding placed on rotor
- Field winding placed on stator
- Starter shunt & series field windings excited
- Voltage in armature windings alternates
- Commutator brush \rightarrow half rectifier
- Current through brushes b/w armature will change direction

Armature windings & Commutation

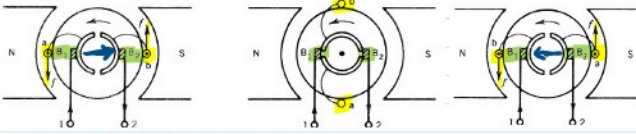

- Current flows $a \rightarrow b$
- Turn shorted \rightarrow to avoid sparking, need min. 3 layers
- Current flows $b \leftarrow a$

Induced voltage: $e_a = \omega_r L_{if} \sin(\omega_r t)$

$$V_a = r_a i_a + \frac{d\lambda}{dt} \rightarrow i_a = 0 \quad \theta_f = \omega_r t$$

$$\lambda_a = L_{aif} i_f + L_{aia} i_a$$

$$e_{arm} \sim \omega \phi_p$$

$$T_{arm} \sim \phi p i_a$$

$$E_a = K_a \omega_r \phi_p$$


$$T_e = K_a \phi_p I_a$$

$$K_a = \text{armature const.}$$

$$E_a = \text{Generated V, back emf}$$

Armature Power: $P_e = E_a I_a = T_e \omega_r = P_m$

Separately Excited DC Machine

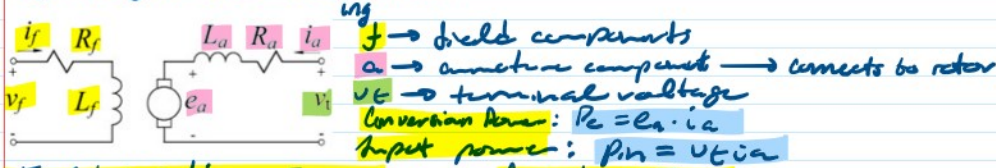

Field windings Eqn

$$V_f = R_f i_f + \left[\frac{d\lambda_f}{dt} \right] \rightarrow V \text{ drop inductor}$$

$$\lambda_f = N_f \phi_p = L_f i_f$$


Armature Eqn

$$V_t = \pm r_a i_a + L_a \left[\frac{di_a}{dt} \right] + e_a$$

$$e_a = K_a \phi_p \omega_r$$

$$T_e = K_a \phi_p i_a$$

Steady State Equivalent ($N \propto L$):

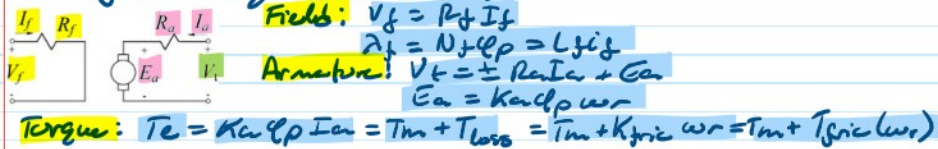

Torque: $T_e = K_a \phi_p I_a = T_m + T_{loss} = T_m + K_f i_f \omega_r = T_m + T_{fric}(\omega_r)$


Torque/Speed const.

- winding flux ϕ_p , Electromagnetic Torque T_e , Back emf e_a
- Mutual inductance b/w field & rotating armature coils

$$L_{af} = K_a \frac{L_f}{N_f} \rightarrow e_a = L_{af} I_f \omega_r$$

$$T_e = \frac{L_{af} I_f I_a}{\lambda \text{ flux linkage}}$$


PM Machines

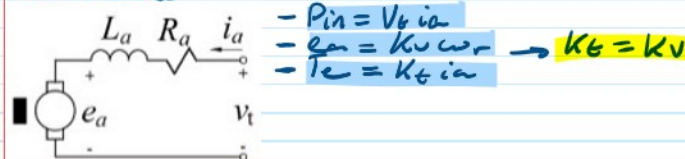

- $P_{in} = V_t i_a$
- $e_a = K_v \omega_r \rightarrow K_t = K_v$
- $T_e = K_t i_a$


Parameters of DC Machine

Locked Rotor Test (DC-Measurements)

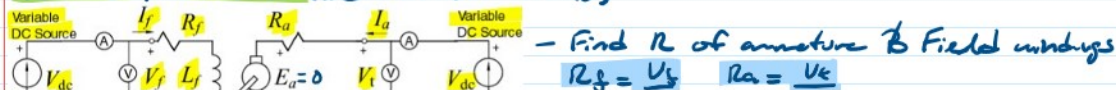

- Find R of armature & Field windings

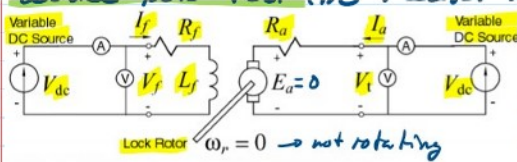
$$R_f = \frac{V_f}{I_f} \quad R_a = \frac{V_a}{I_a}$$



- Find R of armature & Field windings
 $R_f = \frac{V_f}{I_f}$ $R_a = \frac{V_a}{I_a}$

- lock motor, $E_a = 0$

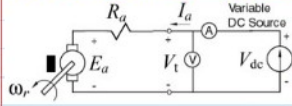No Load Test for PM Motors (Friction vs. Speed)



- knowing R_a , measure I_a , V_a , ω_r

$$V_a = R_a I_a + E_a$$

$$P_e = I_a E_a = \omega_r T_e \rightarrow n(\text{rpm}) \rightarrow \omega(\text{rad/sec}): \omega = \frac{2\pi n}{60}$$


$$T_e = T_{\text{fric}}(\omega_r) = \omega_r K_{\text{fric}}$$

Transient (dynamic)

$$T_{\text{fric}}(\omega_r) = -J \frac{\Delta \omega_r}{\Delta t} = -J \frac{\Delta E_a}{K_v \Delta t}$$

$$J = \frac{T_{\text{fric}}(\omega_r) K_v \Delta t}{\Delta E_a}$$

Open Circuit Test

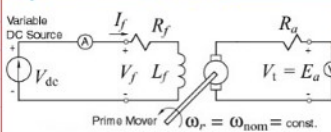


$$E_a = K_v \phi \omega_r = K_v \frac{L_f}{N_f} I_f \omega_r = L_{af} I_f \omega_r = K_v \omega_r$$

$$\phi = \frac{N_f}{N_s} I_f = \frac{L_f}{N_s} I_f$$

Classification of DC Machines

Basic DC Machines

Separately Excited DC Motor

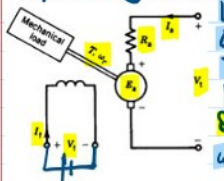

$$V_t = E_a + R_a I_a = I_t R_{\text{load}} = I_a R_{\text{load}}$$

$$E_a = K_v \phi \omega_r = L_{af} I_f \omega_r$$

$$T = K_a \phi I_a = L_{af} I_f I_a$$


$$V_t = R_s I_f$$

Speed Torque Characteristic:

$$\omega_r = \frac{V_t - I_a R_a}{K_v \phi} = \frac{V_t - I_a R_a}{L_{af} I_f} = \left[\frac{V_t}{L_{af} I_f} \right] - \left[\frac{R_a}{L_{af} I_f} \right] I_a$$

NL speed slope

Shunt DC Machine

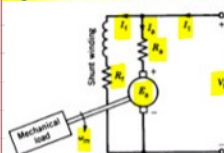


$$L_{af} I_f = \frac{L_{af} V_t}{R_f}$$

Speed Torque Characteristic

$$\omega_r = \frac{V_t}{L_{af} I_f} - \frac{R_a}{L_{af} I_f} I_a = \left[\frac{R_f}{L_{af}} \right] - \left[\frac{R_a R_f^2}{(L_{af} V_t)^2} \right] I_a$$

NL speed slope

Series DC Motor

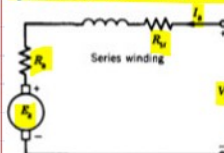

$$V_t = I_a (R_a + R_s) + L_{af} I_a \omega_r$$


$$I_a = \frac{V_t}{R_a + R_s + L_{af} \omega_r}$$

$$T_e = L_{af} I_a^2 = L_{af} I_f I_a$$


Torque Speed Characteristic

$$T = \frac{L_{af} V_t^2}{(R_a + R_s + L_{af} \omega_r)^2}$$

Compound DC Machines

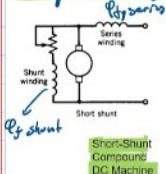

Short-Shunt Compound DC Machine

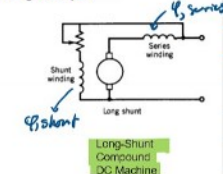


Long-Shunt Compound DC Machine

$$\phi_{\text{total}} = \phi_{\text{shunt}} \pm \phi_{\text{series}}$$


DC Machine Regulation

Speed Regulation (Motors)

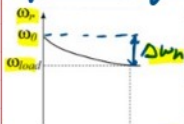


$$\%R = \frac{\omega_{r0} - \omega_{rL}}{\omega_{rL}} \times 100\% = \frac{n_{NL} - n_L}{n_L} \times 100\%$$
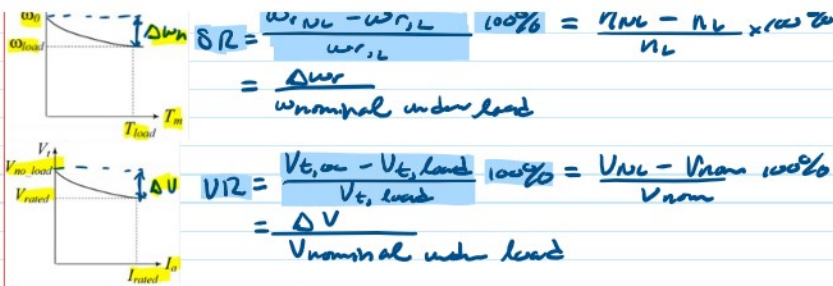
$$= \frac{\Delta \omega_r}{\omega_{rL}}$$



Power Flow & Efficiency

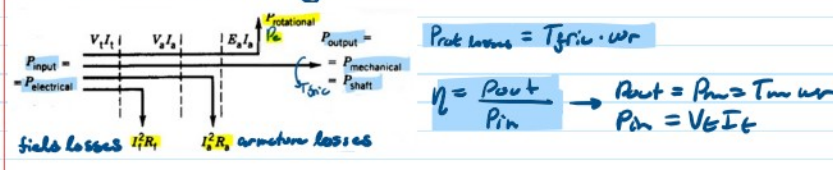

Starting Current

- $I_{a,rated} = \frac{P}{V_t}$
- $I_{a,start} = \frac{V_t - E_a}{R_a} \rightarrow 10 I_{a,start} \gg I_{a,rated} \rightarrow \text{will burn motor!}$

Speed/Torque Control of DC Motors

- Vary Terminal Voltage
 - Vary armature current
- $V_a = r_a i_a + k_v \omega_r$
- $k_v = \text{long } i_g \rightarrow V_a = r_a i_a + k_v \omega_r$
- $T_e = k_v i_a \rightarrow T \text{ control}$
- $\omega_r = \frac{V_a - i_a r_a}{k_v} = \frac{V_a}{k_v} - \frac{r_a}{k_v} T_e \rightarrow \text{speed control}$

Separate

PM

DC-DC Converters for DC-Motors

- DC V source, any V_{out} controlled



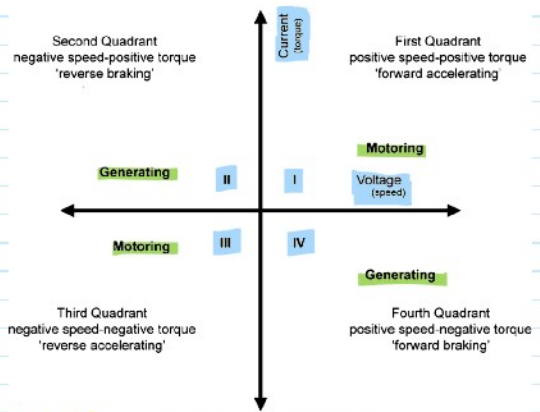
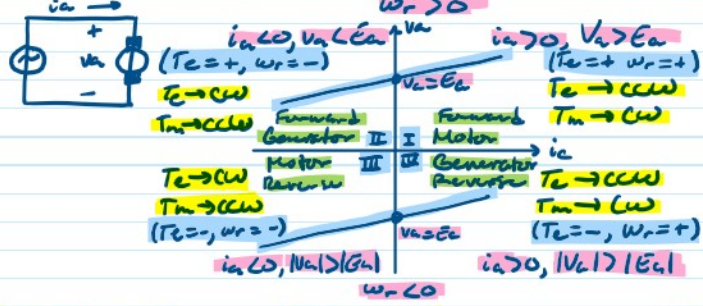


Fig. 1 Four Quadrants of Operation

I-Quadrant

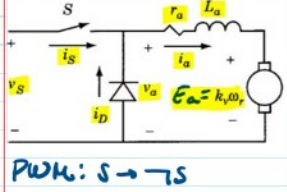

II-Quadrant

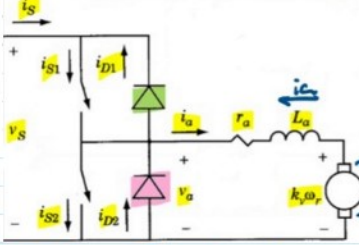

IV-Quadrant

