


AC Circuits

April 20, 2020 7:23 PM


AC Circuit Analysis

Mesh Analysis

ex. Find I_o

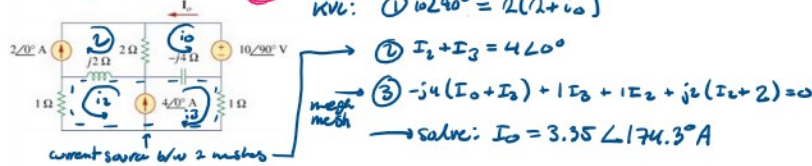

Thvenin & Norton Analysis

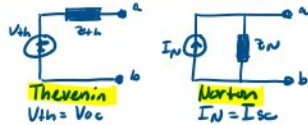

Superposition

- Multiple frequencies involved: solve phasor circuit independently
- Sum of time-domain responses
- Short V sources, Open current sources

Thvenin w/ dependent sources (1A/2A test)

- Finding Thvenin w/ dependent current sources
- Solve KCL w/ 1A source @ terminals for V_a
- Solve KCL w/ 2A source @ terminals for V_b
- Keep dependent & independent sources




Webwork ST1

ST1: Problem 2

Previous Problem Problem List Next Problem

(12 points)

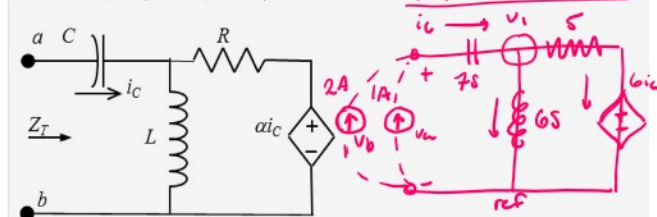Let $R = 5\Omega$, $C = \frac{1}{7}F$, $L = 6H$ and $\alpha = 6V/A$. Determine the requested quantities seen at terminals $a - b$ for an operating frequency of 4rad/s :



Note: In this problem, you may only submit numerical answers. (i.e. if 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

- Impedance: $Z_T = \text{ } \angle \text{ }^\circ \Omega$
- Series-Resistance: $R_T = \text{ } \Omega$
- Series-Reactance: $X_T = \text{ } \Omega$
- Parallel-Conductance: $G_T = \text{ } S$
- Parallel-Susceptance: $B_T = \text{ } S$

