

Two Port Networks

April 23, 2020 11:11 AM

Connecting 2-Port Networks


Cascade



Series



Parallel

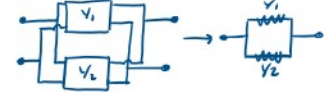

Conversion table

$to \backslash from$	Z	Y	H	G	T
Z	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{y_{22}}{\Delta_y} & -\frac{y_{12}}{\Delta_y} \\ -\frac{y_{21}}{\Delta_y} & \frac{y_{11}}{\Delta_y} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{g_{11}} & -\frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{1}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{11}}{\Delta_t} & \frac{\Delta_t}{\Delta_t} \\ \frac{t_{21}}{\Delta_t} & \frac{1}{\Delta_t} \end{bmatrix}$
Y	$\begin{bmatrix} \frac{y_{22}}{\Delta_y} & -\frac{y_{12}}{\Delta_y} \\ -\frac{y_{21}}{\Delta_y} & \frac{y_{11}}{\Delta_y} \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{1}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_g}{g_{11}} & \frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{1}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{22}}{\Delta_t} & -\frac{\Delta_t}{\Delta_t} \\ \frac{t_{12}}{\Delta_t} & \frac{1}{\Delta_t} \end{bmatrix}$
H	$\begin{bmatrix} \frac{\Delta_h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{1}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_g}{g_{11}} & \frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{1}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{11}}{\Delta_t} & \frac{\Delta_t}{\Delta_t} \\ \frac{t_{21}}{\Delta_t} & \frac{1}{\Delta_t} \end{bmatrix}$
G	$\begin{bmatrix} \frac{1}{g_{11}} & -\frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{1}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_g}{g_{11}} & \frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{1}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_h}{h_{11}} & \frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{1}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{22}}{\Delta_t} & -\frac{\Delta_t}{\Delta_t} \\ \frac{t_{12}}{\Delta_t} & \frac{1}{\Delta_t} \end{bmatrix}$
T	$\begin{bmatrix} \frac{t_{11}}{\Delta_t} & \frac{\Delta_t}{\Delta_t} \\ \frac{t_{21}}{\Delta_t} & \frac{1}{\Delta_t} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{1}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_g}{g_{11}} & \frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{1}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix}$

Port:

- Pair of nodes to connect circuit to
- Current entering a port wire = interaction of voltage & current



Impedance parameters:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Admittance parameters:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Hybrid Parameters:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Inverse Hybrid parameters:

$$\begin{bmatrix} I_1 \\ V_1 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} I_2 \\ V_2 \end{bmatrix}$$

Transmission Parameters:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

Inverse Transmission Parameters:


$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

Connecting 2-Port Networks


Cascade:




Series:

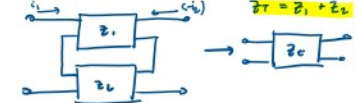

Parallel:

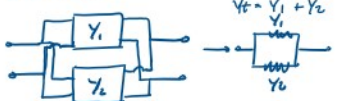


ex. Find parameters Z

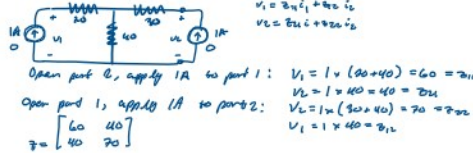

Webwork Two

TWP: Problem 1

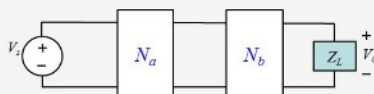(50 points)
 For the individual two-ports shown, the given two-port parameters are known: $\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$
 Note: In this problem, you may only submit numerical answers. (i.e. if 4 is the correct answer, 4 will be marked as correct, but 2-2 will be marked as incorrect.)



a. Determine the transmission and y parameters of the overall two-port. If the y matrix does not exist, contact the teaching staff by private Piazza post to get a different randomized set of parameters.

a) T-Parameters

$$\text{Conversion Matrix: } T_A = \begin{bmatrix} \frac{-\Delta h}{h_{21}} & -\frac{h_{11}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{1}{h_{21}} \end{bmatrix}$$

$$h = \begin{bmatrix} 5 & -6 \\ 6 & -3 \end{bmatrix} \quad \Delta h = -15 - (-36) = 21$$

$$T_A = \begin{bmatrix} -2/6 & -5/6 \\ 1/2 & -1/6 \end{bmatrix}$$

$$\text{Conversion Matrix: } T_B = \begin{bmatrix} \frac{-y_{22}}{y_{21}} & -\frac{1}{y_{21}} \\ \frac{-y_{12}}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{bmatrix}$$

$$y = \begin{bmatrix} 4 & -8 \\ -3 & 6 \end{bmatrix} \quad \Delta y = 56 - 24 = 32$$

$$T_B = \begin{bmatrix} 8/4 & -1/4 \\ -3/4 & 3/4 \end{bmatrix}$$

$$T = T_A \cdot T_B \rightarrow \text{Cascade}$$

b) Y-Parameters

$$\text{Conversion Matrix: } Y_A = \begin{bmatrix} \frac{t_{22}}{t_{12}} & -\frac{\Delta t}{t_{12}} \\ -\frac{1}{t_{12}} & \frac{t_{11}}{t_{12}} \end{bmatrix}$$

$$T = \begin{bmatrix} 2.3333 & -0.4666 \\ 0.714286 & 2.571428 \end{bmatrix} \quad \Delta t = 1.5$$

$$Y = \begin{bmatrix} 1.714285 & 0.571428 \\ 0.714286 & 2.571428 \end{bmatrix}$$

b) Voltage Ratio $G = V_o/V_s \rightarrow Z_L = 6 \Omega$
 - open port 2, Apply 1A to port 1
 - open port 1, Apply 1A to port 2

$$Y\text{-param: } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad Y = \begin{bmatrix} 0.714286 & 2.571428 \\ 1.714285 & 0.571428 \end{bmatrix}$$

a. Determine the transmission and y parameters of the overall two-port. If the y matrix does not exist, contact the teaching staff by private Piazza post to get a different randomized set of parameters.

$[T] = \begin{bmatrix} \text{ } & \text{ } \\ \text{ } & \text{ } \end{bmatrix} \Omega$

$[Y] = \begin{bmatrix} \text{ } & \text{ } \\ \text{ } & \text{ } \end{bmatrix} S$

b. Find the voltage ratio $G = V_2/V_1$ when $Z_L = 6\Omega$.

$G = \text{ } \text{ }$


TWP: Problem 2

Previous Problem Problem List Next Problem

(50 points)

Consider the two-port network shown with $n = 6$, $R = 8k\Omega$ and $C = 3\mu F$.

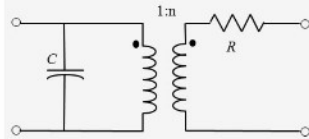
a. Determine the hybrid [h] and impedance [z] parameters (as functions of s ; hint: each hybrid parameter is a first order transfer function).



$[h] = \begin{bmatrix} \text{ } & \text{ } \\ \text{ } & \text{ } \end{bmatrix}$

$[z] = \begin{bmatrix} \text{ } & \text{ } \\ \text{ } & \text{ } \end{bmatrix}$

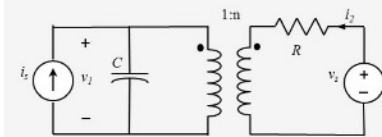
b. For sources $i_s(t) = 3\cos(700t)$ mA and $v_s(t) = 9u(t)$ V, compute $v_1(t)$ and $i_2(t)$ (Hint: use superposition on the result from part (a), using phasor domain analysis for one part and Laplace domain analysis for the other).



[Note: For the sinusoidal portion of the answer, enter angle in radians instead of degrees. Also, for the Heaviside function, use "u(t)"]

$v_1(t) = \text{ } V$

$i_2(t) = \text{ } mA$

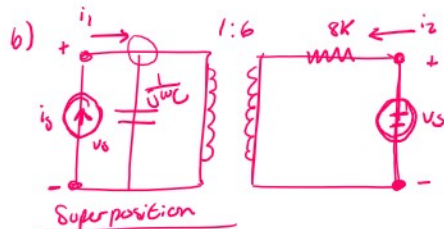

Phasor:

$i_s = 3\cos(700t) \text{ mA}$

$v_s = 9u(t) \text{ V}$

① $I_1 = -6I_2 + V_1(3 \times 10^{-6})s$

② $V_2 = 6V_1 + 8kI_2$

$\rightarrow s = j\omega = j700, I_1 = i_s(t) = 3\cos(700t), V_2 = 0 \rightarrow \text{open port 2}$

① $3 \times 10^{-6} \cos(700t) = -6I_2 + V_1(3 \times 10^{-6})(j700)$

② $0 = 6V_1 + 8kI_2$

$\rightarrow \text{solve } V_1 \text{ \& } I_2:$

$V_1 = 0.604126 \angle -0.486027 \text{ V}, I_2 = 0.4530915 \angle 2.70496 \text{ mA}$

$V_1 = 0.604126 \cos(700t - 0.436627) \text{ V}$

$I_2 = 0.4530915 \cos(700t + 2.70496) \text{ mA}$

Laplace:

$I_1 = 0 \rightarrow \text{open port}$

$V_2 = 9 \text{ (u(t))}$

$y = L \cdot -8 \cdot \Delta y = 56 - 24 = 32$

$T_0 = \begin{bmatrix} 8/4 & -1/4 \\ -3/4 & 7/4 \end{bmatrix}$

$T = T_0 \cdot T_0 \rightarrow \text{descender}$

$T = \begin{bmatrix} -5/8 & -5/8 \\ -1/2 & -1/2 \end{bmatrix} \begin{bmatrix} -3/4 & -1/4 \\ -3/4 & 7/4 \end{bmatrix} = \begin{bmatrix} -0.3333 & -0.58333 \\ 2.3333 & -0.416666 \end{bmatrix}$

- Open port 2, Apply 1A to port 1

- Open port 1, Apply 1A to port 2

Y-param: $I_1 = Y_{11}V_1 + Y_{12}V_2$

$I_2 = Y_{21}V_1 + Y_{22}V_2$

$I_2 = 1.7143V_1 + 0.5714V_2$

$V_2 = -6I_2 \rightarrow I_2 = \frac{-V_2}{6}$

$-\frac{V_2}{6} = 1.7143V_1 + 0.5714V_2$

$-V_2 = 10.2858V_1 + 3.4284V_2$

$\frac{V_2}{V_1} = -2.32269V$


$Y = \begin{bmatrix} 0.714286 & 2.571428 \\ 1.714285 & 0.571428 \end{bmatrix}$



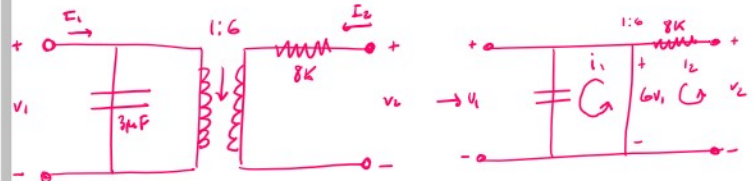a) $\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \rightarrow V_1 = h_{11}I_1 + h_{12}V_2$

$V_2 = 0 \text{ (short port)} \rightarrow h_{11} = \frac{V_1}{I_1} \Omega, h_{21} = \frac{I_2}{I_1}$

$I_1 = 0 \text{ (open port)} \rightarrow h_{12} = \frac{V_1}{V_2}, h_{22} = \frac{I_2}{V_2}$



Transformer:

$n_s V_1 = n_p V_2$

$n_s I_1 = n_p I_2$

① $6V_1 = V_2$

② $-6I_1 = I_2$

③ $V_1 \cdot 2s = I_1$

④ $\frac{V_2}{6k} = I_2$

$\left. \begin{matrix} \text{①} \\ \text{②} \\ \text{③} \\ \text{④} \end{matrix} \right\} \begin{matrix} I_1 = -6I_2 + V_1(3 \times 10^{-6})s \\ V_2 = 6V_1 + 8kI_2 \end{matrix}$

$\begin{bmatrix} I_1 \\ V_1 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$

g-parameters

$g = \begin{bmatrix} (3 \times 10^{-6})s & -6 \\ 6 & 8k \end{bmatrix}$

h-parameters

$h = g^{-1} = \frac{1}{36.024} \begin{bmatrix} 8k & 6 \\ -6 & (3 \times 10^{-6})s \end{bmatrix} = \begin{bmatrix} 222.024 & 0.166555 \\ -0.166555 & 8.32778 \times 10^{-8} \end{bmatrix}$

① $I_1 = -6I_2 + V_1(3 \times 10^{-6})s$

② $V_2 = 6V_1 + 8kI_2$

z-parameters

$V_1 = z_{11}I_1 + z_{12}I_2$

$V_2 = z_{21}I_1 + z_{22}I_2$

$z = \begin{bmatrix} \frac{1}{3 \times 10^{-6}s} & \frac{6}{3 \times 10^{-6}s} \\ \frac{6}{3 \times 10^{-6}s} & \frac{8k}{3 \times 10^{-6}s} + 8k \end{bmatrix}$

Rearrange:

$V_1 = \frac{1}{3 \times 10^{-6}s} I_1 + \frac{6}{3 \times 10^{-6}s} I_2$

$V_2 = 6 \left[\frac{1}{3 \times 10^{-6}s} I_1 + \frac{6}{3 \times 10^{-6}s} I_2 \right] + 8kI_2$

$= \frac{6}{3 \times 10^{-6}s} I_1 + \left(\frac{36}{3 \times 10^{-6}s} + 8k \right) I_2$

expression:

$$I_1 = 0 \rightarrow \text{open port}$$

$$V_2 = q(u(t))$$

$$\textcircled{1} 0 = -6 I_2 + V_1 (3 \times 10^{-6}) S$$

Laplace
determine $\textcircled{2} \frac{q}{s} = 6 V_1 + 8 k I_2$

→ solve V_1 & I_2 :

$$V_1 = \frac{6}{2.6666 \times 10^{-3} s + 4 s} \rightarrow \mathcal{L}^{-1}\{V_1\} = \left[6(-0.25 e^{-1500t} + 0.25) \right] u(t) \text{ V}$$

$$I_1 = \frac{3 \times 10^{-6}}{2.6666 \times 10^{-3} s + 4} \rightarrow \mathcal{L}^{-1}\{I_1\} = \left[0.001125 e^{-1500t} \right] u(t) \text{ mA}$$

Superposition

$$V_1 = 0.604122 \cos(700t - 0.436627) + \left[6(-0.25 e^{-1500t} + 0.25) \right] u(t)$$

$$I_1 = 0.4530915 \cos(700t + 2.70496) + \left[0.001125 e^{-1500t} \right] u(t)$$