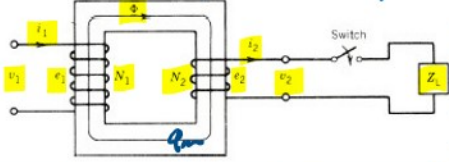


2. Transformers

Tuesday, October 27, 2020 3:47 AM

2.1 Ideal Transformer


- winding $R = 0$
- leakage flux & core losses = 0
- permeability of core $\mu \rightarrow \infty \therefore$ not muf to establish flux in core = 0



Voltage induced $e_1 = v_1 = N_1 \frac{d\Phi}{dt}$
 $e_2 = v_2 = N_2 \frac{d\Phi}{dt}$
 $\frac{v_1}{v_2} = \frac{N_1}{N_2} = a \rightarrow \text{turn ratio}$

- inst. power in = inst. power out $N_1 i_1 = N_2 i_2$
 $v_1 i_1 = v_2 i_2 \therefore$ no power losses
 $\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{1}{a}$


2.1.1 Impedance Transfer

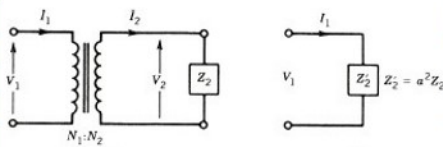

Primary: $Z_1 = Z_2 a^2 = Z_2'$
 Secondary: $Z_2' = \frac{1}{a^2} Z_1$

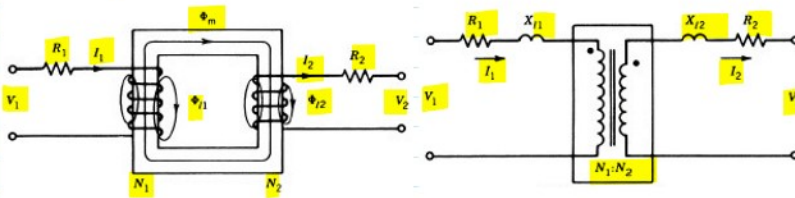2.2 Practical Transformer


- winding resistances
- permeability core $\mu \neq \infty$
- core losses
- windings link \neq same flux



- Mutual flux Φ_m in core
- leakage flux Φ_l links single winding, varies w/ current

Leakage inductance: $L_{l1} = \frac{N_1^2 \Phi_{l1}}{i_1}$, $L_{l2} = \frac{N_2^2 \Phi_{l2}}{i_2}$
 $\Phi_1 = \Phi_{l1} + \Phi_m = \frac{N_1 i_1}{R_{l1}} + \frac{N_1 i_1 - N_2 i_2}{R_m}$
 $\Phi_2 = \Phi_{l2} - \Phi_m = \frac{N_2 i_2}{R_{l2}} - \frac{N_2 i_2 - N_1 i_1}{R_m}$
 $\lambda_1 = N_1 \Phi_1 = L_{l1} i_1 + L_{m1} i_1 - L_{m2} i_2 \rightarrow L = \frac{N^2}{R}$
 $\lambda_2 = N_2 \Phi_2 = L_{l2} i_2 + L_{m2} i_2 - L_{m1} i_1$
 $L_{m1} = L_{m2}$

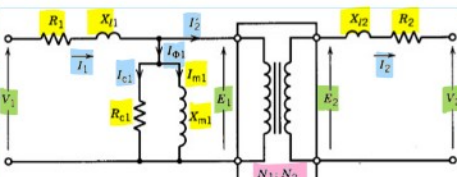2.2.1 Determination of equivalent circuit parameters




$R_{c1} \rightarrow$ core losses

$I_1' = I_2 \frac{N_2}{N_1} = \frac{I_2}{a}$

$X_{m1} = L_{m1} \omega \rightarrow$ magnetizing reactance


- Referred to primary:

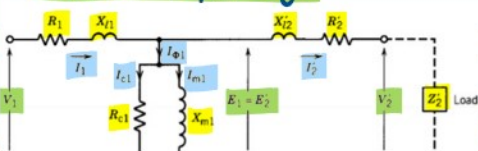

$R_2' = R_2 \left(\frac{N_1}{N_2} \right)^2 = R_2 a^2$

$X_{l2}' = X_{l2} \left(\frac{N_1}{N_2} \right)^2 = X_{l2} a^2$

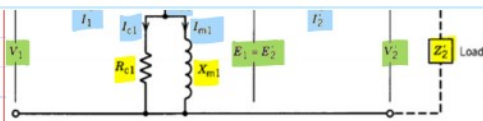$I_{\phi 1} \rightarrow$ Exciting current




$$X'_{L2} = X_{L1} (\overline{N_2}) = X_{L1} a^2$$

$I_{e1} \rightarrow$ Exciting current
 $I_{m1} \rightarrow$ Magnetizing current

Scaled Secondary values: $V'_2 = V_2 a$ $X'_{L2} = X_{L1} a^2$
 $I'_2 = \frac{I_2}{a}$ $R'_2 = R_2 a^2$
 $Z'_2 = Z_2 a^2$

- Referred to secondary:

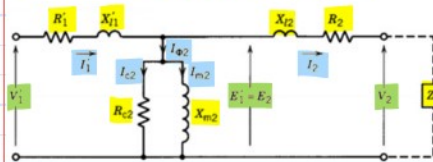

Scaled Primary values:

$$V'_1 = \frac{V_1}{a} \quad X'_{L1} = \frac{X_{L1}}{a^2} \quad X_{m2} = \frac{X_{m1}}{a^2}$$

$$I'_1 = I_1 a \quad R'_1 = \frac{R_1}{a^2} \quad R_{L2} = \frac{R_{L1}}{a^2}$$



Transformer Rating

- ex. 10KVA, 1100/110 V \rightarrow voltage windings & turn ratios
 \rightarrow KVA rating: each winding designed for 10KVA
 \therefore current rating = $10000/1100 = 9.09$ A flows in 110V windings
 $= 10000/110 = 90.9$ A flows in 1100 V windings
- Primary winding carries excitation current (I_{e1}) (rated current)

Tests for Determination of Parameters

Open Circuit Test (No load Test)

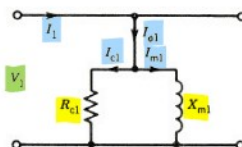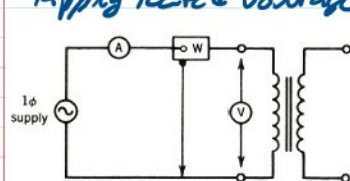- Apply voltage to HV or LV
- Secondary winding is open
- Apply Rated Voltage, Measure V_{oc} , I_{e1} , P_{oc}



$$P_{oc} = \frac{V_{oc}^2}{R_c}$$



$$I_c = \frac{V_{oc}}{R_c}$$

$$X_{m1} = \frac{V_{oc}}{I_{m1}}$$

$$I_{oc}^2 = I_m^2 + I_c^2 \quad I_m = \sqrt{I_{oc}^2 - I_c^2}$$

Short Circuit Test

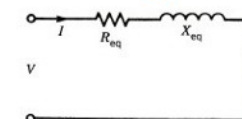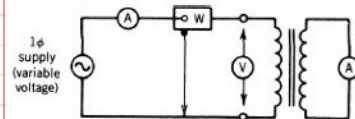- Short circuit one winding
- Apply rated current to other winding, Measure V_{sc} , I_{sc} , P_{sc}



$$P_{sc} = I_{sc}^2 R_{eq}$$


$$Z_{eq} = \frac{V_{sc}}{I_{sc}} = \sqrt{R_{eq}^2 + X_{eq}^2}$$

$$X_{eq} = X_{L1} + a^2 X_{L2} \quad X_{L1} = X_{L2} = \frac{X_{eq}}{2}$$

$$R_{eq} = R_1 + a^2 R_2 \quad R_1 = R_2 = \frac{R_{eq}}{2}$$

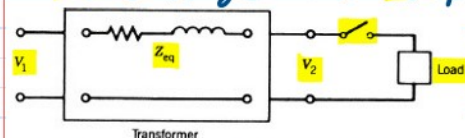2.3 Voltage Regulation

- Secondary load designed to operate @ const. V
- Load V changes due to V drop in internal impedance (core losses)



w/o secondary load: $V_2|_{NL} = \frac{V_1}{a}$
w/ secondary load: $V_2|_L = V_2|_{NL} \pm \Delta V_2$

- Load terminal V neg $\uparrow \downarrow$ depending on load nature
- $\uparrow \Delta V_2$ undesirable \therefore want $\downarrow Z_{eq}$ internal impedance
- Voltage Regulation: identify characteristic of ΔV_L w/ loading
 $\rightarrow \Delta |V_L|$ as load current changes from no-load \rightarrow loaded

$$\text{Voltage Regulation} = \frac{|V_2|_{NL} - |V_2|_L}{|V_2|_L}$$

\rightarrow Calculate w/ equivalent primary/secondary circuits

$$\text{Primary side: } VR = \frac{|V_2|_{NL} - |V_2|_L}{|V_2|_L}$$

\therefore Load voltage \rightarrow rated voltage $|V_2|_L = |V_2|_{rated}$

$$V_1 = V_2 + I_2 R_{eq1} + j I_2 X_{eq1}$$

\therefore load voltage \rightarrow rated voltage $|V_2|_L = |V_2|_{\text{rated}}$
 $V_1 = V_2' + I_2' R_{eq1} + j I_2' X_{eq1}$

If no load ($I_1 = I_2 = 0$): $|V_2'|_{NL} = V_1$

$$\therefore \text{VR \%} = \frac{|V_1| - |V_2'|}{|V_2'|_{\text{rated}}} \times 100\%$$

2.4 Efficiency

- Since transformers = static, \downarrow losses, $\sim 99\%$ efficiency
 $\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{P_{\text{out}}}{P_{\text{in}} + P_{\text{losses}}} = \frac{P_{\text{out}}}{P_{\text{in}} + P_c + P_{cu}} \rightarrow P_c$ core loss
 P_{cu} copper loss


- Find P_{cu} w/ winding currents & their resistances

$$P_{cu} = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{eq1} = I_2^2 R_{eq2}$$

- P_c depends on peak flux density of core \rightarrow depends on V_{in}

$P_c \sim \text{const.}$, Find using No Load test
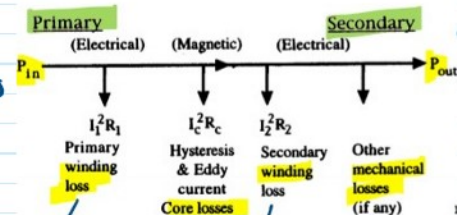
$$P_{\text{out}} = V_2 I_2 \cos \theta_2$$



2.4.1 Maximum Efficiency

- @ const. V_2 & load PF θ_2 , Max efficiency @ $\frac{d\eta}{dI_2} = 0$

- Conditions: $P_c = I_2^2 R_{eq2}$

Core loss = Copper loss


Full load: $P_{cu,FL} = I_{2,FL}^2 R_{eq2}$

Condition \rightarrow rated

- @ const. V_2 & load current I_2 , max η :

$$\frac{d\eta}{d\theta_2} = 0 \rightarrow \theta_2 = 0, \cos \theta_2 = 1$$

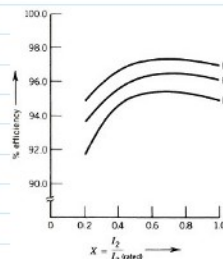\therefore Max efficiency @ PF=1 (resistive)
 @ load current $\rightarrow P_{cu} = P_c$




2.5 Autotransformer

- Variable AC voltage obtained @ secondary

- Primary & secondary connected

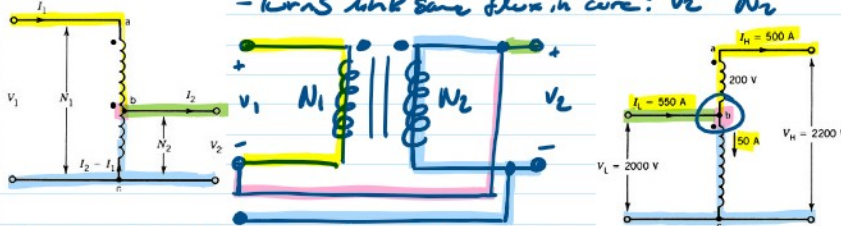- Turns don't share flux in core: $\frac{V_1}{N_1} = \frac{V_2}{N_2} = a$



- To compute KVA as autotransformer:

\rightarrow Find current rating of windings $\rightarrow I = \frac{\text{KVA}}{V}$

\rightarrow Terminal currents for full load $\rightarrow I_H, I_L$



$$\rightarrow \text{KVA: } \text{KVA}_L = \frac{V_L \times I_L}{a} \quad \text{KVA}_H = \frac{V_H \times I_H}{a}$$

2.6 Three Phase Transformers

- Required to step up/step down voltages in power transmission

Y-Y Connection

Y-Y connection

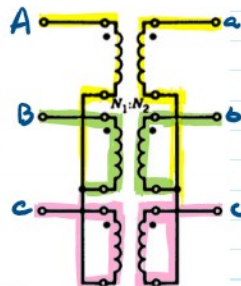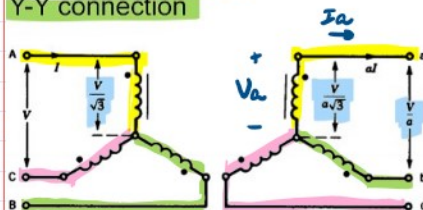


- Rarely used


- Problems exciting currents & induced voltages

Y-Δ Connection

Y-Δ connection

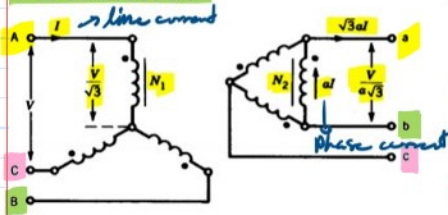

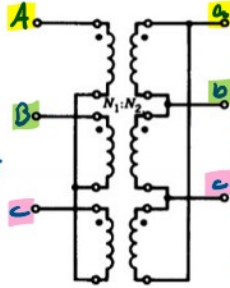
- Neutrals should be grounded on the primary




- Used to step down HV → LV
- Neutral pt. on HV can be grounded

Δ-Y Connection

Δ-Y connection

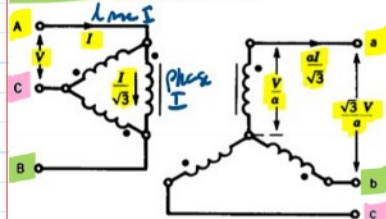

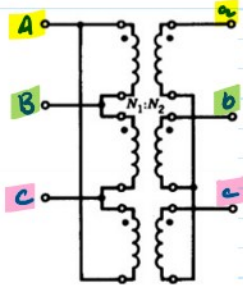
- Neutrals may be grounded on the secondary




- Step up Voltage
- $P_{\text{source}} = (I_A \cdot V_{AB})/3$
- $P_{\text{load}} =$

Δ-Δ Connection

Δ-Δ connection

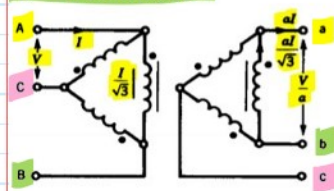


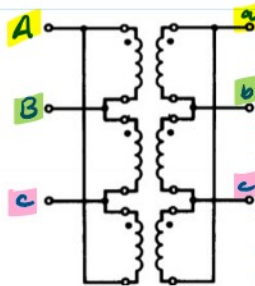
- No phase shift of line voltages
- One transformer can be removed



- one transformer can be removed if remaining 2 can deliver 3-phase power @ 58% of original rating

Open-Δ Connection

Open-Δ connection

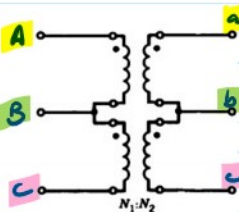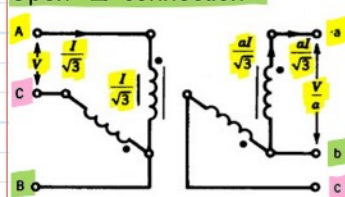



- Open Δ / V connection
- 58% of original 3-phase rating

- Voltages same as Δ-Δ
- line current smaller

Single Phase Equivalent circuits & Phase Shift

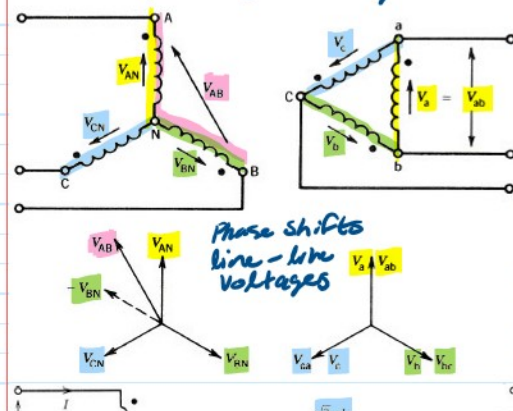- Y-Δ & Δ-Y provide 30° phase shift b/w line-line Voltage
- V_{AN} & V_{ab} aligned
- V_{AB} leads V_{ab} by 30°
- Δ-Δ & Y-Y → no phase shifts




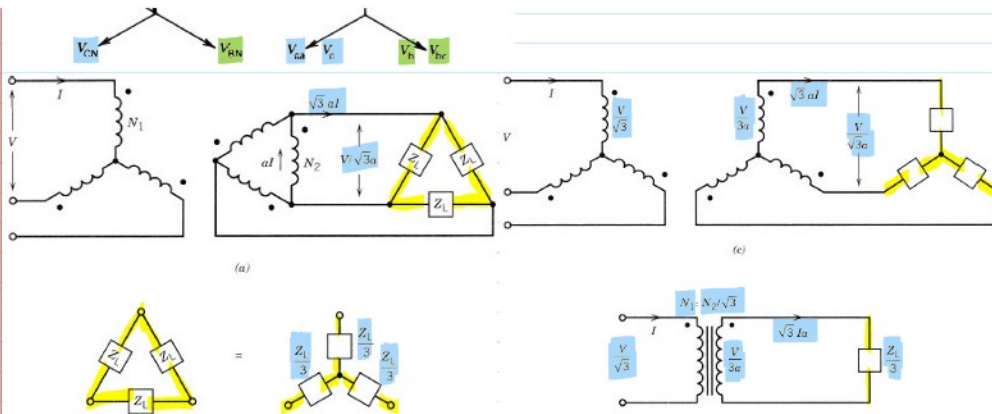

- Turn Ratio a' of Y-Y equivalent transformer: $a' = \frac{V/\sqrt{3}}{V/\sqrt{3}a} = \sqrt{3}a$

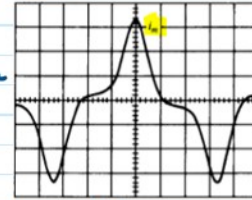2.7 Harmonics in Transformers

- \uparrow flux density \rightarrow \downarrow magnetic material
- \therefore Transformer is designed to operate in saturation region of core
 - \rightarrow exciting current \rightarrow non-sinusoidal
 - \rightarrow will contain fundamental & odd harmonics




- @ V_{rated} , 3rd Harmonic in exciting current = 5-10% of fundamental
- @ V_{rated} , 3rd Harmonic current = 30-40% of fundamental

Inrush Current in Transformer

- Exciting current normally \downarrow $\leq 5\%$ I_{rated}
- when transformer connected to power system, \uparrow inrush current flows during transient period \rightarrow 10-20% \times I_{rated}
- Important to determine Max Mech. stress in windings & protective system


Supply $v = \sqrt{2}V \sin \omega t = N \frac{d\phi}{dt} \rightarrow$ neglect core losses & winding R
 $\phi = \frac{1}{N} \int v dt$

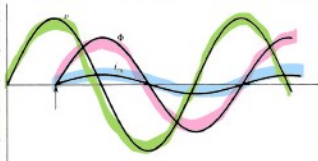- Case 1: Transformer connected when $V @ \text{Max}$




- No Transient in flux
- $\phi = \phi_{max} \sin(\omega t - 90^\circ)$ for $\omega t > 90^\circ$
- $\phi_{max} = \frac{\sqrt{2}V}{\omega N}$
- No inrush current, system in steady state

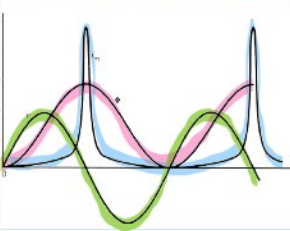- Case 2: Transformer connected when $V @ 0$



$\phi = \frac{\sqrt{2}V}{N} \int_0^t \sin \omega t dt = \frac{\sqrt{2}V}{\omega N} (1 - \cos \omega t) = \phi_{max} - \phi_{max} \cos \omega t$

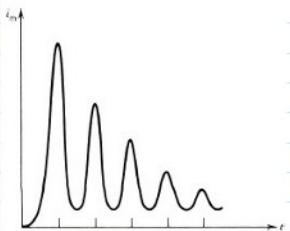- Peak flux doubled, \uparrow peak magnetizing current \therefore core saturation
- \therefore winding resistance, inrush current decays rapidly



- Effects of winding resistance on inrush current

2.8 Per-Unit (PU) System

- Select Base Values, convert params to PU
- Calculate & convert back to original units

2.8 Per-Unit (PU) System

- Select Base Values, convert params to PU
- Calculate & convert back to original units

$$\text{Quantity (PU)} = \frac{\text{Actual Value}}{\text{Base Value}}$$

Per-Unit for Single Phase

- Select Base power S_{base} & Base Voltage V_{base}
- Calculate Base current & Impedance


$$V_{base} = R \cdot I_{base} \quad R_{pu} = \frac{R}{Z_{base}} = R \frac{I_{base}}{V_{base}} = R \frac{I_{base}^2}{S_{base}}$$

- Transformation from one base \rightarrow Another

$$\text{Quantity (base 2)} = \text{Quantity (base 1)} \frac{\text{Value Base 1}}{\text{Value Base 2}}$$

$$V_{pu}(\text{base 2}) = V_{pu}(\text{base 1}) \frac{V_{base 1}}{V_{base 2}} \quad I_{pu}(\text{base 2}) = I_{pu}(\text{base 1}) \frac{I_{base 1}}{I_{base 2}}$$
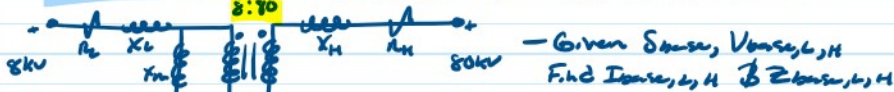
$$Z_{pu}(\text{base 2}) = Z_{pu}(\text{base 1}) \frac{Z_{base 1}}{Z_{base 2}} = Z_{pu}(\text{base 1}) \frac{S_{base 2} (V_{base 1})^2}{S_{base 1} (V_{base 2})^2}$$



divide by 8kV divide by 80kV

\therefore scale both sides 1:1

$$a = \frac{8kV}{80kV} = \frac{1}{10}$$

- Calculate Per-Unit:

$$R_{L,pu} = \frac{R_L}{Z_{base,L}} \quad X_{L,pu} = \frac{X_L}{Z_{base,L}}$$

$$R_{H,pu} = \frac{R_H}{Z_{base,H}} \quad X_{H,pu} = \frac{X_H}{Z_{base,H}}$$

$$X_{m,pu} = \frac{X_m}{Z_{base,L}}$$

- Per-unit Equivalent Circuit:

