

# 2nd Order Circuits

April 23, 2020 11:12 AM

Laplace transform:

Inductor:

$$v(t) = L \frac{di(t)}{dt} \rightarrow V(s) = sLI(s) - Li_L(0)$$



Capacitor:

$$\int i(t) dt \rightarrow \frac{I(s)}{s} + \frac{\int_{-\infty}^0 i_L(t) dt}{s}$$

$$v(t) = \frac{1}{C} \int i(t) dt \rightarrow V(s) = \frac{I(s)}{sC} + \frac{v_C(0)}{sC}$$



★ Webwork ST4

ST4  
Problem 8  
User Settings  
Grades


## ST4: Problem 8

Previous Problem Problem List Next Problem

(8 points)


For the circuit shown below, let  $I = 4u(t)A$ ,  $C = 0.7F$ ,  $R = 50\Omega$ ,  $L = 9H$  and  $I_1 = 11A$ . Find:

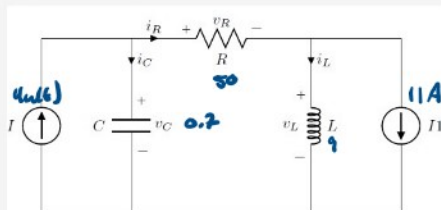- (a)  $i_L(0^+)$ ,  $v_C(0^+)$ ,  $v_R(0^+)$   
 (b)  $\frac{di_L(0^+)}{dt}$ ,  $\frac{dv_C(0^+)}{dt}$ ,  $\frac{dv_R(0^+)}{dt}$   
 (c)  $i_L(\infty)$ ,  $v_C(\infty)$ ,  $v_R(\infty)$



**Note:** In this problem, you may only submit numerical answers. (i.e. If 4 is the correct answer, 4 will be marked as correct, but 2+2 will be marked as incorrect.)

$i_L(0^+)$	<input type="text"/>	$\frac{di_L(0^+)}{dt}$	<input type="text"/>	$i_L(\infty)$	<input type="text"/>
	A		A/S		A
$v_C(0^+)$	<input type="text"/>	$\frac{dv_C(0^+)}{dt}$	<input type="text"/>	$v_C(\infty)$	<input type="text"/>
	V		V/S		V
$v_R(0^+)$	<input type="text"/>	$\frac{dv_R(0^+)}{dt}$	<input type="text"/>	$v_R(\infty)$	<input type="text"/>
	V		V/S		V

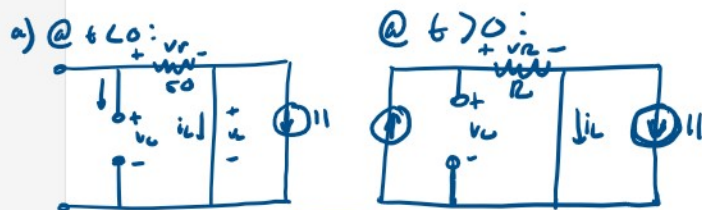

$$\begin{aligned} i_L(0^+) &= i_L(0^-) = -11A \\ v_C(0^+) &= v_C(0^-) = 0V \\ v_R(0^+) &= v_R(0^-) = 0V \end{aligned}$$

Capacitor



$$\begin{aligned} i &= C \frac{dv}{dt} \\ v &= \frac{1}{C} \int_{-\infty}^t i dt \end{aligned}$$

$$v_C(0^+) = v_C(0^-)$$

Inductor

$$\begin{aligned} v &= L \frac{di}{dt} \\ i &= \frac{1}{L} \int_{-\infty}^t v dt \end{aligned}$$

$$i_L(0^+) = i_L(0^-)$$

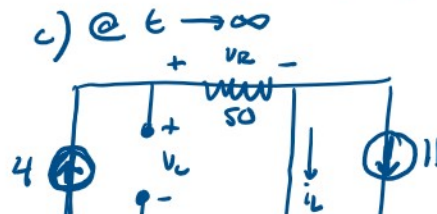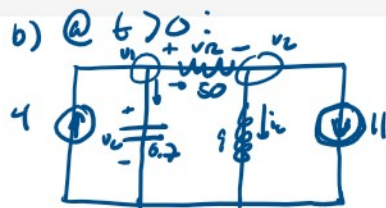



$$\text{KCL1: } 4 = i_C + i_R$$

$$4 = C \frac{dv_L}{dt} + \frac{v_R}{R}$$

$$\frac{dv_L(0^+)}{dt} = \frac{4}{0.7}$$

$$= 5.71429 \text{ V/s}$$


$$\text{KCL2: } L \frac{di_L}{dt} = v_L - 0$$

$$\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{9}$$

$$= 0 \text{ A/s}$$

$$\text{KCL3: } R i_R = v_L$$

$$v_R(0^+) = 0 \text{ V/s}$$

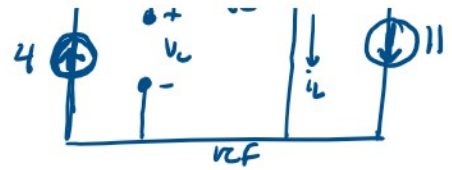

$$v_R(\infty) = 4.50$$

$$= 200 \text{ V}$$

$$v_C(\infty) = v_R(\infty) = 200 \text{ V}$$

$$i_L(\infty) = 4 - 11$$

$$= -7 \text{ A}$$